


PAPER 3

1. (a) State the voltage current relationships for (i) resistance
(ii) inductance and (iii) capacitance.

Solution Refer Sections 1.5, 1.6 and 1.7.

- (b) Two coupled coils with self inductances $L_1=0.8\text{H}$ and $L_2=0.2\text{H}$ have a coupling coefficient of 0.6 has 500 turns. If the current in coil 1 is $I_1(t) = 10 \sin 200t$; determine the voltage at coil 2 and the maximum flux set up by the coil 1.

Solution

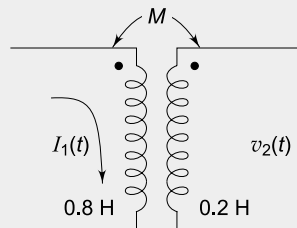

$$\begin{aligned} M &= K\sqrt{L_1 L_2} \\ &= 0.6\sqrt{0.8 \times 0.2} \\ &= 240 \text{ mH} \end{aligned}$$

The voltage across the coil 2 $v_2(t) = \pm M \frac{di_1(t)}{dt}$

$$v_2(t) = \frac{d}{dt}(10 \sin 200t)$$

$$v_2(t) = 2000 \text{ C is } 200t \text{ volts}$$

- (c) A torroid is made of steel rod of 2 cm diameter. The mean radius of torroid is 20 cm relative permeability of steel is 2000. Compute the current required to produce 1 m web of flux and 1000 turns in the torroid.

Solution Length of the flux path $= \pi D = \pi \times 20 = 62.83 \text{ cm} = 0.6283 \text{ m}$

$$\text{Area of flux path} = \frac{\pi}{4} d^2 = \frac{\pi}{4} (2)^2 = 3.141 \text{ cm}^2$$

$$\text{Magnetic field intensity } H = \frac{B}{\mu_o \mu_r}$$

$$B = \frac{\phi}{\text{Area}} = \frac{10^{-3}}{3.141 \times 10^{-4}} 3.1 \text{ web / m}^2$$

$$H = \frac{3.1}{4\pi \times 10^{-7} \times 2000} = 1233.45 \text{ AT / m}$$

$$\begin{aligned} mmf &= H \times l = 1233.45 \times 0.6283 \\ &= 775 \text{ A.T.} \end{aligned}$$

$$\begin{aligned}\text{Exciting current} &= \frac{\text{mmf}}{T} \\ &= \frac{775}{1000} = 0.775 \text{ A}\end{aligned}$$

2. (a) If $I_1 = 10 \angle 0^\circ$, $I_2 = 20 \angle 60^\circ$ and $I_3 = 12 \angle -30^\circ$ find $I_1 + I_2 + I_3$.

$$\begin{aligned}\text{Solution} \quad I_1 + I_2 + I_3 &= 10 \angle 0^\circ + 20 \angle 60^\circ + 12 \angle -30^\circ \\ &= 30.392 + j11.32 \\ &= 32.432 \angle 20.429^\circ\end{aligned}$$


- (b) Prove that the form factor for a sinusoidal current wave form is 1.11.

Solution Refer Section 4.4.7.

3. (a) Derive an expression for resonance frequency of a series R-L-C circuit.

Solution Refer Section 8.1.

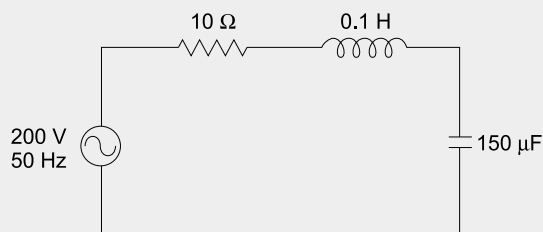- (a) A coil of resistance 10Ω and an inductance of 0.1 H is connected in series with a capacitor of capacitance $150 \mu\text{F}$ across a 200 V , 50 Hz supply. Calculate (i) Impedance (ii) Current (iii) Power and power factor of the circuit



Solution (i) Total impedance

$$\begin{aligned}Z &= R + j\omega L - \frac{j}{\omega c} \\ &= 10 + j31.45 - j21.22 \\ &= 10 + j10.194 \\ &= 14.279 \angle 45.55^\circ\end{aligned}$$

$$\begin{aligned}\text{(ii) Current } I &= \frac{V}{Z} \\ &= \frac{200 \angle 0^\circ}{14.279 \angle 45.55^\circ} \\ &= 14 \angle -45.55^\circ\end{aligned}$$

$$\begin{aligned}\text{(iii) Power factor} &= \cos (45.55^\circ) \\ &= 0.7 \text{ lagging}\end{aligned}$$

E.14*Network Analysis*


$$\begin{aligned}
 \text{Real power} &= VI \cos \phi \\
 &= 200 \times 14 \times 0.7 \\
 &= 1.9 \text{ kW} \\
 \text{Reactive power} &= VI \sin \phi \\
 &= 200 \times 14 \times \sin (-45.55) \\
 &= -1.998 \text{ KVAR}
 \end{aligned}$$

“-1” Sign indicates that it absorbs the reactive power.

4. (a) Define cut set and tie set

Solution Refer Sections 2.7 and 2.8.

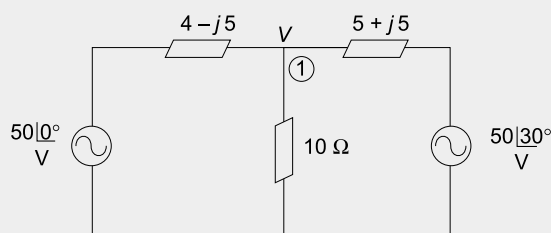- (b) Determine the current in the 10Ω resistor in the circuit shown in the figure below.




Solution Apply nodal analysis at point (1), we get


$$\begin{aligned}
 \frac{V - 50\angle 0^\circ}{4 - j5} + \frac{V}{10} + \frac{V - 50\angle 30^\circ}{5 + j5} &= 0 \\
 V \left[\frac{1}{4 - j5} + \frac{1}{10} + \frac{1}{5 + j5} \right] &= \frac{50\angle 0^\circ}{4 - j5} + \frac{50\angle 30^\circ}{5 + j5} \\
 V [0.297 + j0.0219] &= 11.708 + j4.267 \\
 V [0.298\angle 4.219^\circ] &= 12.46\angle 20.02^\circ \\
 \Rightarrow V &= 41.812 \angle 15.801^\circ
 \end{aligned}$$

$$\begin{aligned}
 \text{Current through the } 10 \Omega \text{ resistor } I_{10} &= \frac{V}{R} \\
 &= \frac{41.812 \angle 15.801^\circ}{10} \\
 &= 4.1812 \angle 15.80^\circ \text{ Amp}
 \end{aligned}$$

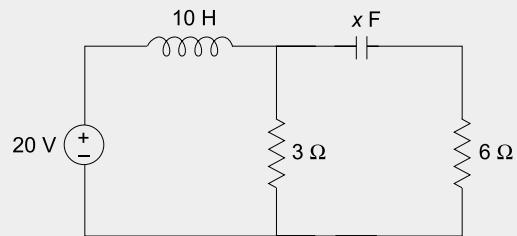
5. Draw the dual network for the given network as in the following figure.




Solution

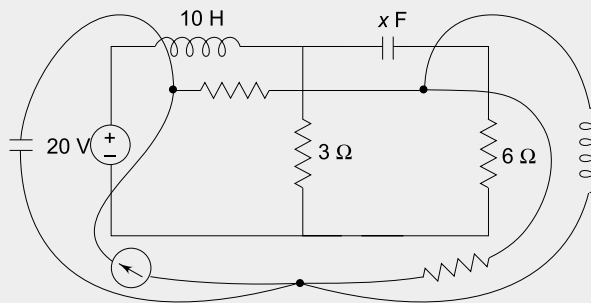

Dual network

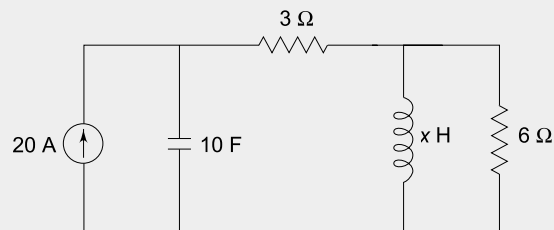

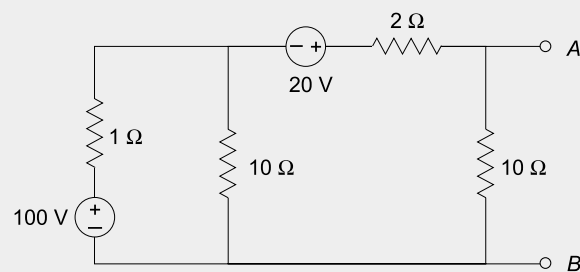
6. (a) Obtain the Norton's equivalent circuit at the terminals A, B for the following figure.



For finding the Norton's resistance, replace the voltage sources by the short circuit.

E.16

Network Analysis

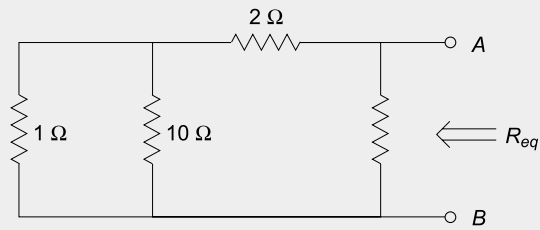


$$R_{eq} = \{[(1 \parallel 10) + 2] \parallel 10\}$$

$$= 2.253 \, \Omega$$

For finding the I_N short the terminals A and B and find current I_N . Apply superposition


(i) with 100 V source

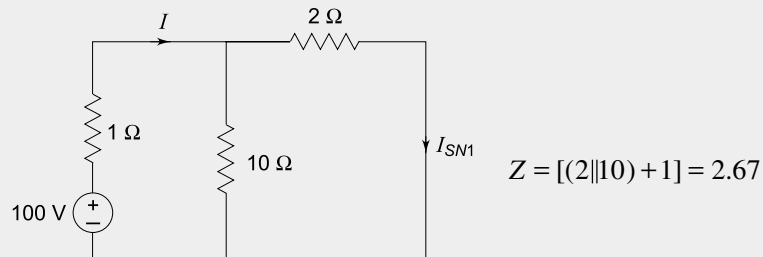

$$\text{Total current } I = \frac{100}{Z}$$

$$= \frac{100}{2.67} = 37.45 \, \text{A}$$

(ii) With 20 V source

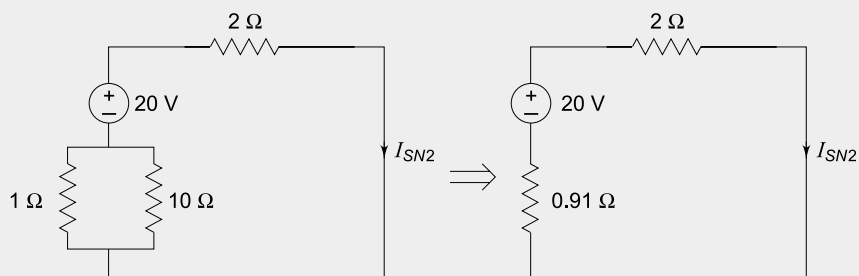


$$I_{SN2} = \frac{20}{2.91} = 6.872 \, \text{A}$$

$$\therefore I_{SN} = I_{SN1} + I_{SN2}$$


$$= 31.21 + 6.872$$

$$= 38.08 \, \text{A}$$

∴ Nortons equivalent circuit is given by

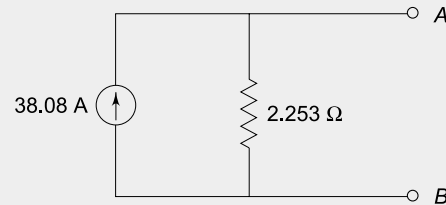

(b)

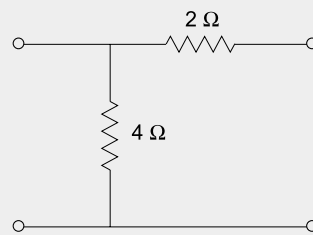

For the 2 port network, find h -parameters.

Solution We know that

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$\therefore h_{11} = \frac{1.33I_1}{I_1} = 1.33\Omega$$


$$h_{21} = -\frac{4}{6} \frac{I_1}{I_1} = -0.66$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{12} = \left. \frac{I_{21}}{V_2} \right|_{I_1=0}$$


$$h_{22} = \frac{I_2}{6I_2} = 0.166v$$

$$V_1 = 4I_2$$

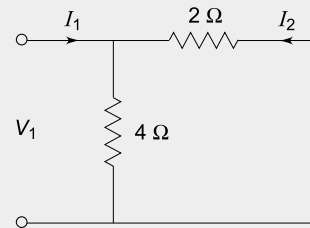

$$\begin{aligned} V_1 &= (2 \parallel 4)I_1 \\ &= 1.33 I_1 \\ I_2 &= -I_1 \times \frac{4}{6} \end{aligned}$$


If $I_1 = 0$

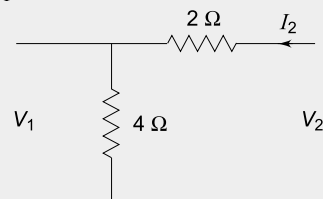

$$h_{12} = \frac{4I_2}{6I_2} \quad V_2 = 6I_2$$

$$= 0.66$$

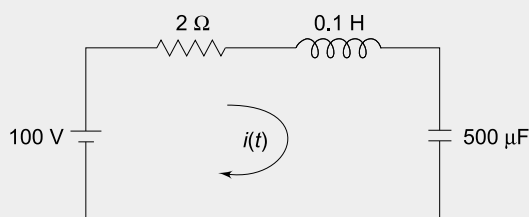7. A series RLC circuit with $R = 5 \Omega$, $L = 0.1 \text{ H}$ and $C = 500 \mu\text{F}$ has a D.C. voltage of 100 V applied at $t = 0$ through a switch. Find the resulting current transient.



Solution $5i(t) + 0.1 L \frac{di(t)}{dt} + \frac{1}{500 \times 10^{-6}} \int i(t) dt = 100$

$$\frac{d^2 i}{dt^2} + 50 \frac{di}{dt} + 2000 = 0$$

$$D^2 + 50D + 2000 = 0$$

$$D = -25 \pm j37.08$$

$$\therefore i(t) = e^{-25t} [K_1 \cos 37.08t + K_2 \sin 37.08t] \quad (1)$$

1st initial condition is that current through the inductor cannot change instantaneously.

Also voltage drop across capacitor cannot change instantaneously

Hence at $t = 0^+$

$$\frac{di}{dt}(0^+) = \frac{V_o}{L} = \frac{100}{0.1} = 1000$$

Substituting initial conditions $i(0^+) = 0$

$$\therefore 0 = K_3$$

On differentiating equation (1), we get

$$\frac{di}{dt} = e^{-25t} [-37.08 K_1 \sin 37.08t + 37.08 K_2 \cos 37.08t]$$

$$-25e^{-25t} (K_1 \cos 37.08t + K_2 \sin 37.08t)$$

$$= e^{-25t} [\sin 37.08t (-37.08 K_1 - 25 K_2) + \cos 37.08t (37.08 K_2 - 25 K_1)]$$

$$\frac{di}{dt}(0^+) = 37.08 K_2 - 25 K_1$$

$$\Rightarrow K_2 = \frac{1000}{37.08} = 26.96$$

$$\therefore i(t) = e^{-25t} (26.96 \sin 37.08t)$$

8. (a) Explain Dot convention.

Solution Refer Section 9.4.

8. (b) Explain briefly about the locus diagrams.

Solution Refer Section 8.6.