

## PAPER 6

1. (a) Explain KCL and KVL.


*Solution*

Refer Sections 1.12 and 1.9 (Chapter 1)

1. (b) A capacitor is charged to 1 volt at  $t = 0$ . A resistor of 1 ohm is connected across its terminals. The current is known to be of the form  $i(t) = e^{-t}$  amperes for  $t > 0$ . At a particular time the current drops to 0.37A at that instant determine.
- At what rate is the voltage across the capacitor changing?
  - What is the value of the charge on the capacitor?
  - What is the voltage across the capacitor?
  - How much energy is stored in the electric field of the capacitor?
  - What is the voltage across the resistor?

*Solution*

Refer Problem 11.3 (Chapter 11).

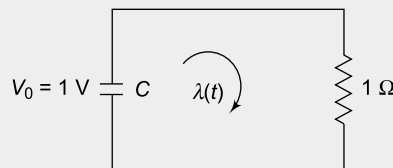

The current equation is

given as  $i(t) = i(0^+) e^{-t/RC}$ ; given  $i(t) = e^{-t/RC}$

$$i(0^+) = 1 \text{ A}; RC=1; C=1\text{F}$$

When  $i(t)=0.37$  amperes

$$i(t) = 0.37 = e^{-t/1}$$

$$-t \log_e e = \log_e 0.37$$

$$t = 0.9942 \text{ sec}$$

$$i(t) = C \frac{dV(t)}{dt} \Rightarrow \frac{dV(t)}{dt} = \frac{i(t)}{C} = \frac{0.37}{1} = 0.37 \text{ V/sec}$$

$$\text{or } V_i(t) = \frac{1}{C} \int_0^t i(t) dt + V_0$$

$$= -\frac{1}{C} \int_0^t e^{-t} dt + V_0 \quad [\because i(t) = - \dot{V}(t)]$$

$$= \frac{-1}{1} \frac{e^{-t}}{(-1)} + 1 = e^{-t}$$

$$V_c(t) = e^{-t} \text{ for } t > 0$$

$$\therefore \frac{dV_c(t)}{dt} = -e^{-t} = -e^{-0.9942} = -0.37 \text{ V/sec}$$

(ii) Charge on the capacitor

$$Q = C V_c = 1 \cdot e^{-t} = 0.37 \text{ coulombs}$$

(iii) Voltage across the capacitor

$$V_c(t) = e^{-t} = 0.37 \text{ volts}$$

(iv) Energy stored in the capacitor

$$W_c = \frac{1}{2} C V_c^2 = \frac{1}{2} 1 (e^{-t})^2 = \frac{e^{-2t}}{2} = 0.06845 \text{ joules}$$

(v) Voltage across the resistor at  $t = 0.9942$  sec

$$V_R = i(t) \cdot R = e^{-t} = 0.37 \text{ V}$$

2. (a) Define Magneto Motive Force (MMF); reluctance, and flux density in a magnetic circuit. Specify the units of each of the above quantities.

*Solution*

Refer Section 9.11 (Chapter 9).

2. (b) Explain “dot convention” for a set of magnetically coupled coils. A cast steel electromagnet has an air gap of length 2 mm and an iron path of length 30 cms. Find the MMF needed to produce a flux density of 0.8T in the air gap. The relative permeability of the steel core at this flux density is 1000. Neglect leakage and fringing.

*Solution*

For “dot convention” refer Section 9.4 (Chapter 9).

Refer Example 10.2 (Chapter 10).

$$\text{Air-gap length } l_g = 2 \text{ mm} = 2 \times 10^{-3} \text{ m}$$

$$\text{Iron path length } l_i = 30 \text{ cm} = 30 \times 10^{-2} \text{ m}$$

$$\text{Flux density } B = 0.8 \text{ T} = 0.8 \text{ Wb/m}^2$$


$$\mu_r = 1000$$

$$\text{Total A.T} = \text{mmf} = H_i l_i + H_g l_g$$

$$\begin{aligned} & \frac{B \times l_i}{\mu_0 \mu_r} + \frac{B}{\mu_0} l_g \\ &= \frac{0.8 \times 30 \times 10^{-2}}{4\pi \times 10^{-7} \times 1000} + \frac{0.8 \times 2 \times 10^{-3}}{4\pi \times 10^{-7}} \\ &= 1464 \text{ A.T.} \end{aligned}$$

Hence, total MMF required to produce a flux density of 0.8T = 1464 AT.

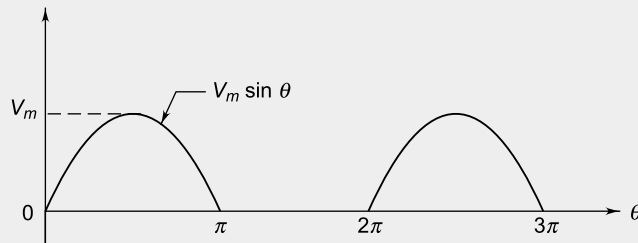3. (a) Find R.M.S. and average value of the following waveform.




*Solution*

Refer problem 4.13 (Chapter 4)

$$\begin{aligned} \text{R.M.S. value, } V_{\text{r.m.s.}} &= \sqrt{\frac{1}{2\pi} \int_0^\pi V_m^2 \sin^2 \theta \, d\theta} \\ &= \sqrt{\frac{V_m^2}{2\pi} \int_0^\pi \frac{(1 - \cos 2\theta)}{2} \, d\theta} \\ &= \sqrt{\frac{V_m^2}{4\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^\pi} \\ &= \frac{V_m}{2} \end{aligned}$$

$$\begin{aligned} \text{Average value, } V_{\text{ave}} &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \theta \, d\theta = \frac{V_m}{2\pi} [-\cos \theta]_0^{2\pi} \\ &= \frac{V_m}{\pi} \end{aligned}$$

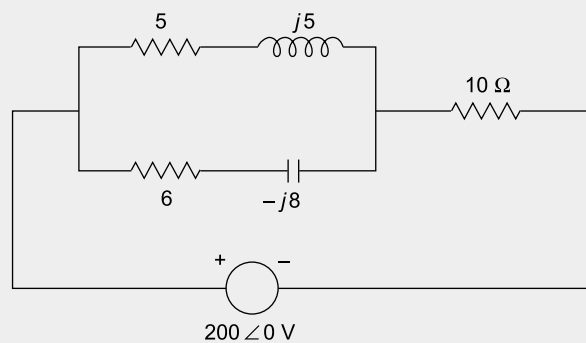3. (b) Find the total current and the power consumed by the circuit.



*Solution*

Total impedance of the circuit,

$$Z_T = (5 + j5) \parallel (6 - j8) + 10$$

$$Z_T = 16.15 + j0.769$$

$$I = \frac{V}{Z} = \frac{200 \angle 0}{16 + 5 + j0.769} = 12.35 - j0.588 \text{ A}$$

$$= 12.36 \angle -2.72^\circ$$

Power consumed  $= I^2 R$

$$= (12.36)^2 \times 16.15 = 2467 \text{ W}$$

or  $VI \cos \theta = 200 \times 12.36 \times \cos (-2.72) = 2467 \text{ W}$ .


4. (a) For a series RL circuit obtain the locus of current as inductance is changed from 0 to  $\infty$  when the applied voltage is constant.

*Solution*

Refer Section 8.1(b) (Chapter 8)

4. (b) Obtain the  $z$ -parameters of the following two-ports network.

Two-port network

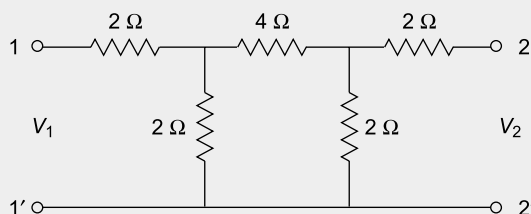

*Solution*

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{6 \times 2}{6 + 2} + 2 = 3.5 \Omega$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{6 \times 2}{6 + 2} + 2 = 3.5 \Omega$$


$$z_{12} = \left. \frac{V_1}{I_1} \right|_{I_1=0} = \frac{\frac{I_2 \times 2}{6 + 2} \times 2}{I_2} = 0.5 \Omega$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{\frac{I_1 \times 2}{6 + 2} \times 2}{I_1} = 0.5 \Omega$$

The parameters of the network are

$$z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 3.5 & 0.5 \\ 0.5 & 3.5 \end{bmatrix}$$

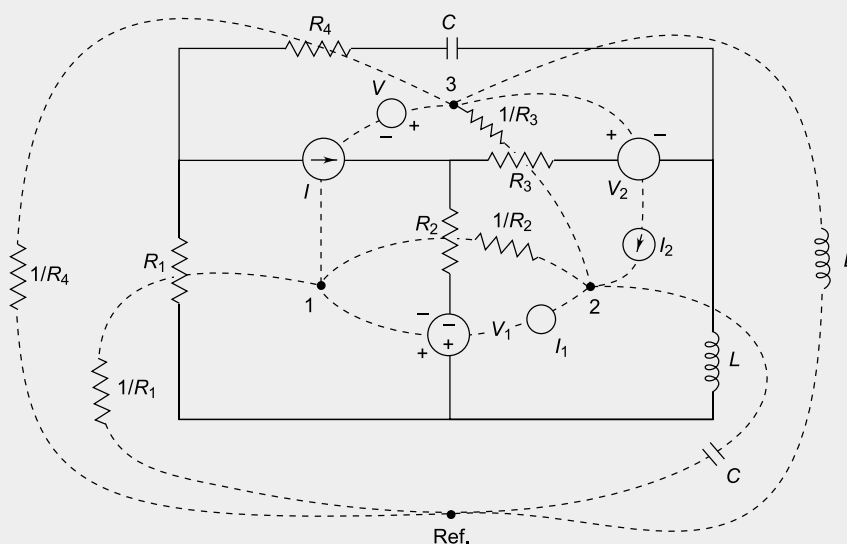5. What is duality? Explain the procedure for obtaining the dual of the given planar network shown below.




*Solution*

Refer Section 3.8 (Chapter 3)

**Rule 1** If a voltage source in the original network produces a c.w. current in the mesh, the corresponding dual element is a current source whose direction is towards node representing the corresponding mesh.

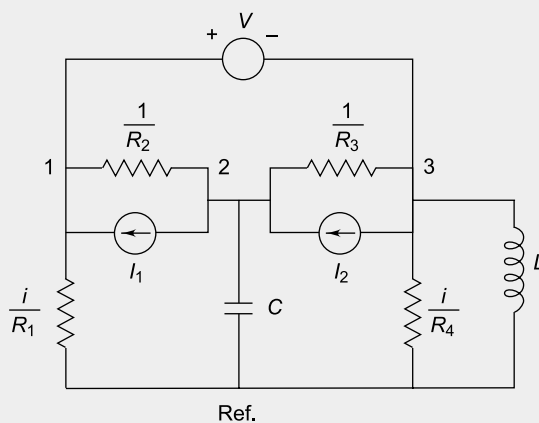**Rule 2** If a current source in the original network produces a current in clockwise direction in the mesh, the voltage source in the dual network will have a polarity such that the node representing the corresponding mesh is positive.




Dual of the planar circuit given in 6(a).

# E.44

## Network Analysis

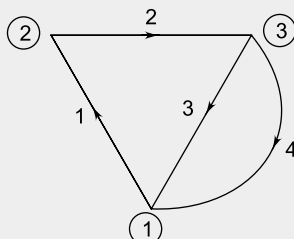6. (a) Construct the incident matrix for the graph show in figure.



*Solution*

Refer Section 2.4 (Chapter 2)

The dimensions of incidence matrix 'A' is  $n \times b$  where  $n$  is number of nodes and  $b$  is number of branches, hence the dimensions of the incidence matrix for the above graph is  $3 \times 4$ .

Incidence matrix

$n$  — nodes


$b$  — branches

$$A = \begin{array}{c|cccc} & \begin{array}{c} p \\ n \end{array} & 1 & 2 & 3 & 4 \\ \hline 1 & 1 & 0 & -1 & -1 \\ 2 & -1 & 1 & 0 & 0 \\ 3 & 0 & -1 & 1 & 1 \end{array}$$

The incidence matrix is given by

$$A = \begin{bmatrix} 1 & 0 & -1 & -1 \\ -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix}$$

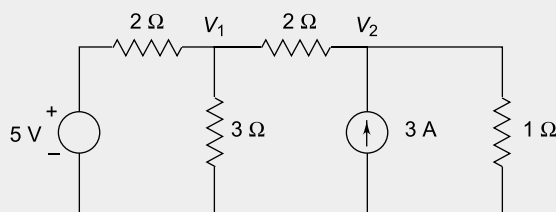6. (b) Use nodal analysis, to determine the voltage  $V_1$  and  $V_2$  in the circuit shown.



*Solution*

Refer Section 2.12 (Chapter 2).

The nodal equation for the two nodes are

$$\frac{V_1 - 5}{2} + \frac{V_1}{3} + \frac{V_1 - V_2}{2} = 0 \quad \dots 1$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} = 3 \quad \dots 2$$

From 1  $1.333 V_1 - 0.5 V_2 = 2.5$

From 2  $-0.5 V_1 + 1.5 V_2 = 3$

Solving the above equations for  $V_1$  and  $V_2$  yields


$$V_1 = 3 \text{ V and } V_2 = 3 \text{ V.}$$

7. (a) State and explain the Thevenin's theorem? State for what type problems this theorem is useful.

*Solution*

Refer Section 3.3 (Chapter 3).

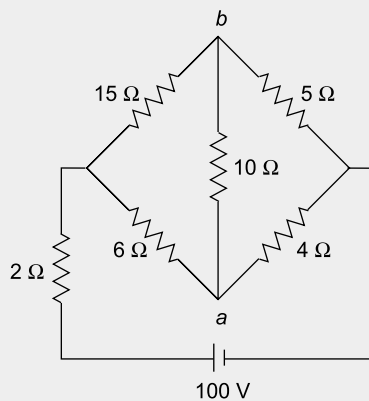
7. (b) Find the current through  $10 \Omega$  resistor using Thevenin's theorem.



*Solution*

Refer Problem 3.6 (Chapter 3).

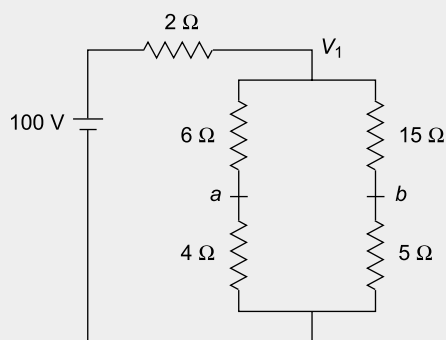Let us redraw the circuit by removing  $10\Omega$ .



Applying KCL at  $V_1$

$$\frac{V_1 - 100}{2} + \frac{V_1}{10} + \frac{V_1}{20} = 0$$

# E.46



## Network Analysis

from which

$$V_1 = 76.92 \text{ V}$$

$$V_{th} = V_a - V_b$$

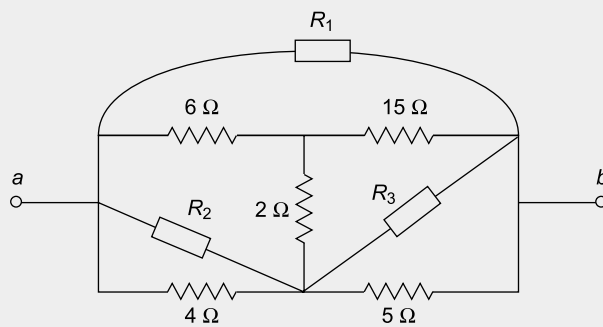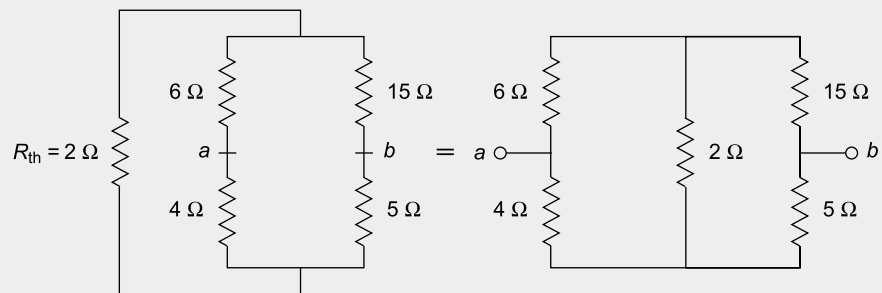
$$= \frac{V_1}{6+4} \times 4 - \frac{V_1}{15+5} \times 5 = 11.538 \text{ V}$$



$$R_1 = \frac{6 \times 15 + 15 \times 2 + 2 \times 6}{2} = 66$$

$$R_2 = \frac{132}{15} = 8.8$$


$$R_3 = \frac{132}{6} = 22$$

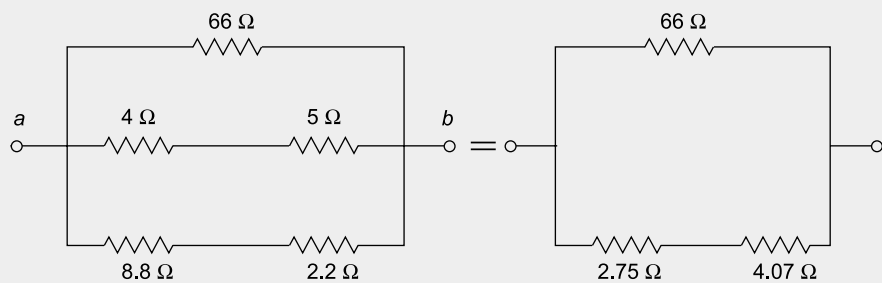



$$R_{ab} = R_{th} = \frac{66 \times 6.82}{72.82} = 6.184 \Omega$$

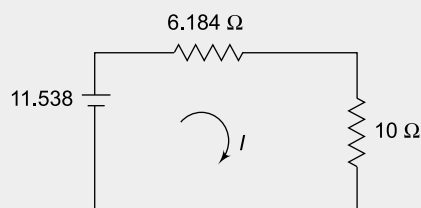Thevenin's equivalent circuit is given by




$$\text{where } I = \frac{11.538}{16.184} = 0.7129 \text{ A}$$

8. (a) For R-L-C series circuit with d.c. excitation discuss the under-damped, over-damped and critically damped cases.

*Solution*

Refer Section 11.4 (Chapter 11).

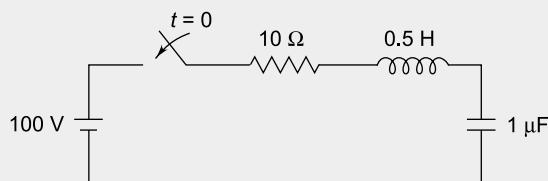8. (b) Obtain the current  $i(t)$  for  $t \geq 0$  using time domain approach.



*Solution*

Refer Example 11.3 (Chapter 11).

Writing KVL for the above circuit.

$$100 = 10i + 0.5 \frac{di}{dt} + \frac{1}{1 \times 10^{-6}} \int i dt$$

Differentiating w.r.t.  $t$

$$0 = 10 \frac{di}{dt} + 0.5 \frac{d^2i}{dt^2} + 10^6 i$$

$$\frac{d^2i}{dt^2} + 20 \frac{di}{dt} + 2 \times 10^6 i = 0$$

$$(D^2 + 20D + 2 \times 10^6)i = 0 \text{ where } D = \frac{di}{dt}$$

$$D_1, D_2 = \frac{-20 \pm \sqrt{400 - 4 \times 2 \times 10^6}}{2}$$

$$D_1 = -10 + j1414; D_2 = -10 - j1414$$

The roots are in the form of  $-K_1 \pm jK_2$

Therefore the solution for the current is given by

$$i(t) = e^{-k_1 t} [C_1 \cos k_2 t + C_2 \sin k_2 t]$$

$$i(t) = e^{-10t} [C_1 \cos 1414 t + C_2 \sin 1414 t]$$

Substitute the initial conditions to find  $C_1$  and  $C_2$

At  $t = 0$ ; the current following through the circuit is zero.

$$i = 0 = 1 [C_1 \cos 0 + C_2 \sin 0]$$

$$C_1 = 0$$

$$i(t) = e^{-10t} C_2 \sin 1414t.$$

$$\frac{di(t)}{dt} = C_2 [e^{-10t} 1414 \cos 1414 t + e^{-10t} (-10) \sin 1414t]$$

At  $t = 0$ , the voltage across the inductor

$$L \frac{di(t)}{dt} = 100$$

$$\frac{di(t)}{dt} = 200$$

$$200 = C_2 e^{-(10 \times 0)} 1414$$

$$C_2 = 0.1414$$

The equation for current is given by

$$i(t) = e^{-10t} (0.1414 \sin 1414 t)$$

$$i(t) = 0.1414 e^{-10t} \sin 1414t$$