

Complex Impedance

1. A 250 V, 50 Hz voltage is applied to a coil of inductance 5 H and resistance of $2\ \Omega$ in series with a capacitance C . What value must ' C ' have in order that the voltage across the coil shall be 280 V. Draw the phasor diagram.

Solution:

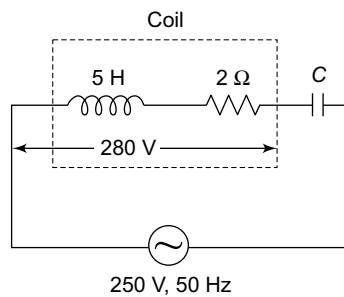


Fig. 5.1

Impedance of the coil $Z_{\text{coil}} = R + j\omega L$

$$Z_{\text{coil}} = 2 + j_{2\pi} \times 50 \times 5 = 2 + j1570$$

$$Z_{\text{coil}} = 2 + j1570 \approx 1570 \angle 90^\circ$$

Voltage across the coil is

$$V_{\text{coil}} = 280\text{ V}$$

$$I = \frac{280}{1570 \angle 90^\circ} = 0.178 \angle -90^\circ$$

Total impedance $Z_T = \frac{V}{I} = \frac{250}{0.178 \angle -90^\circ} = j1404.5\ \Omega$

$$\begin{aligned}
 Z_{\text{capacitance}} &= Z_T - Z_{\text{coil}} \\
 &= j1404.5 - j1570 \\
 &= -j165.5 \, \Omega
 \end{aligned}$$

$$\therefore X_C = -j165.5$$

$$\frac{1}{\omega C} = -j165.5 \text{ and } C = 192 \, \mu\text{F}$$

$$\frac{1}{2\pi \times 50 \times C} = -j165.5$$

Phasor diagram

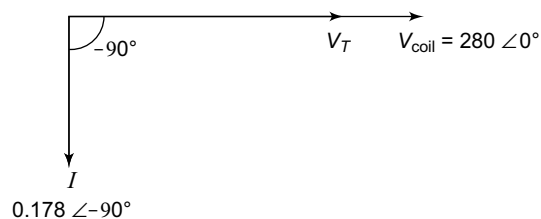


Fig. 5.2

2. Find the values of R and C in the circuit shown so that $V_b = HV_a$ and V_a and V_b are in phase quadrature.

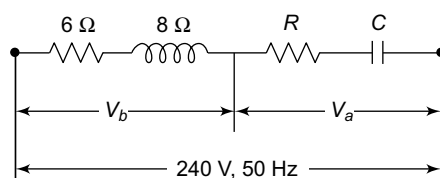


Fig. 5.3

Solution: Consider applied voltage to the circuit is $240 \angle 0^\circ$ volts

Total voltage applied

$$V_a + V_b = 240 \angle 0^\circ$$

$$V_a + 4V_a = 240$$

$$V_a = \frac{240}{5} = 48 \text{ volts}$$

Since the current flowing through all the elements is the same, we have

$$\begin{aligned}\frac{V_b \angle 0^\circ}{6 + j8} &= \frac{V_a \angle -90^\circ}{R - jX_C} \\ R - jX_C &= \frac{(6 + j8) V_a \angle -90^\circ}{V \angle 0^\circ} \\ &= \frac{(6 + j8) 48 \angle -90^\circ}{4 \times 48 \angle 0^\circ} \\ &= 2.5 \angle -36.9^\circ \\ R - jX_C &= (2 - j1.5) \Omega\end{aligned}$$

$$\therefore R = 2 \Omega \quad \frac{1}{\omega C} = 1.5$$

$$X_C = 1.5 \Omega \quad \frac{1}{2\pi \times 50 \times C} = 1.5$$

$$\therefore C = 2.12 \times 10^{-3} \text{ F}$$

3. The applied voltage to a series circuit is $v = 50 \sin(2000t - 25^\circ)$ volts and the resultant current through the circuit is $i = 8 \sin(2000t + 5^\circ)$ amps. Find the circuit elements.

Solution: The effective applied voltage

$$V_{\text{rms}} = \frac{50}{\sqrt{2}} \angle -25^\circ \text{ Volts}$$

The effective current in the circuit

$$I_{\text{rms}} = \frac{8}{\sqrt{2}} \angle 5^\circ \text{ ampers.}$$

The phasor diagram is

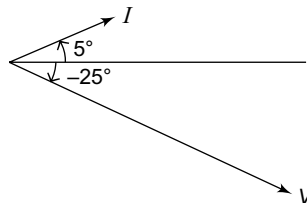


Fig. 5.4

Phase angle between voltage and current is 30° leading.

$$\text{The impedance } Z = \frac{V}{I} = \frac{(50/\sqrt{2}) \angle -25^\circ}{(8/\sqrt{2}) \angle 5^\circ} = 6.25 \angle -30^\circ \Omega$$

$$Z = 6.25 \angle -30^\circ = 5.412 - j3.125$$

$$= R - jX_C$$

$$\therefore R = 5.412$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2000 \times C} = 3.125$$

$$C = \frac{1}{2000 \times 3.125} = 160 \times 10^{-6} \text{ F}$$

4. For the parallel circuit shown below, find the branch currents and the total current and construct the phasor diagram.

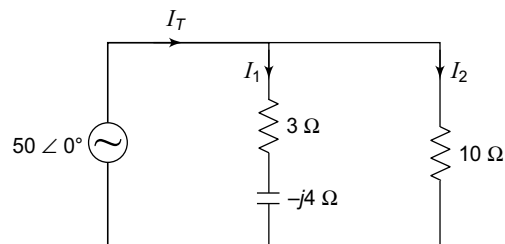


Fig. 5.5

Solution: The current through $(3 - j4) \Omega$ is

$$I_1 = \frac{50 \angle 0^\circ}{3 - j4} = \frac{50 \angle 0^\circ}{5 \angle -53.1^\circ}$$

$$I_1 = 10 \angle 53.1^\circ \text{ amp} = (6 + j8) \text{ amp}$$

The current through 10Ω is

$$I_2 = \frac{50 \angle 0^\circ}{10} = 5 \angle 0^\circ \text{ amp.} = 5 \text{ amp.}$$

Total current

$$\begin{aligned} I_T &= I_1 + I_2 \\ &= 6 + j8 + 5 = 11 + j8 \end{aligned}$$

$$I_T = 13.6 \angle 36^\circ \text{ amp.}$$

The phasor diagram

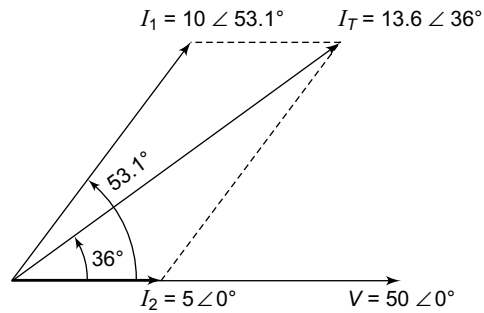


Fig. 5.6

5. A three-element series circuit contains one inductance $L = 0.02$. The applied voltage and resulting currents are shown on the phasor diagram. If $\omega = 500$ rad/sec, what are the two circuit elements?

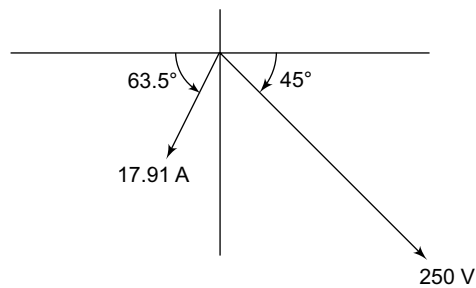


Fig. 5.7

Solution: The voltage applied to the circuit

$$V = 250 \angle -45^\circ \text{ volts}$$

The current through the circuit $I = 7.91 \angle -116.5^\circ$

$$\text{The total impedance } Z = \frac{V}{I} = \frac{250 \angle -45^\circ}{7.91 \angle -116.5^\circ}$$

$$Z = 31.60 \angle 71.5^\circ \Omega$$

$$Z = (10 + j30) \Omega$$

Since the angle of the impedance is positive. The circuit is an RL circuit

$$\begin{aligned} \therefore Z &= R + j(X_{L1} + X_{L2}) \\ &= 10 + j\omega(L_1 + L_2) \end{aligned}$$

$$= 100 + j500 (L_1 + L_2)$$

Equating reactive parts, we get

$$500 (L_1 + L_2) = 30$$

$$L_1 + L_2 = \frac{30}{500} = 0.06 \text{ H}$$

$$L_1 = 0.02 \text{ H}$$

$$L_2 = 0.04 \text{ H}$$

6. The total current entering the parallel circuit shown in the figure is given by $I_T = 18 \angle 45^\circ \text{ A}$. Determine the potential difference between points A and B.

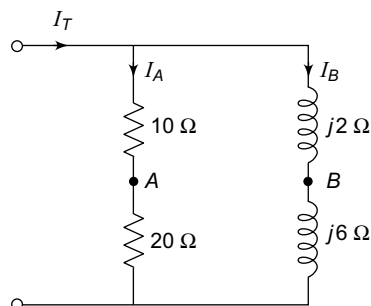


Fig. 5.8

Solution: Total current in the circuit $I_T = 18 \angle 45^\circ \text{ A}$

Current in 30Ω branch
$$I_A = I_T \frac{Z_B}{Z_A + Z_B}$$

$$I_A = \frac{18 \angle 45^\circ \times j8}{30 + j8} = 4.66 \angle 120^\circ \text{ A}$$

and current in $j8 \Omega$ branch
$$I_B = I_T \frac{Z_A}{Z_A + Z_B}$$

$$I_B = \frac{18 \angle 45^\circ \times 30}{30 + j8} = 17.5 \angle 30^\circ \text{ A}$$

The voltage across 20Ω resistance is

$$V_{20} = V_A (20) = 4.66 \times 20 \angle 120^\circ$$

$$= 93.2 \angle 120^\circ \text{ V}$$

The voltage across $j6 \Omega$ is

$$V_{j6} = I_B (j6) = 17.5 \angle 30^\circ \times 6 \angle 90^\circ$$

$$= 105 \angle 120^\circ \text{ V}$$

\therefore Voltage across terminals AB

$$V_{AB} = V_{20} - V_{j6} = 93.2 \angle 120^\circ - 105 \angle 120^\circ$$

$$V_{AB} = 11.8 \angle -60^\circ \text{ V}$$

7. A series circuit has $R = 8 \Omega$ and $C = 30 \mu\text{F}$. At what frequency will the current lead the voltage by 30° ?

Solution: The impedance of the circuit

$$Z = R - jX_C = \sqrt{R^2 + X_C^2} \left[\tan^{-1} \left(-\frac{X_C}{R} \right) \right]$$

$$-30^\circ = \tan^{-1} \left(\frac{-X_C}{R} \right)$$

$$\frac{-X_C}{R} = \tan(-30^\circ) = -0.577$$

$$\frac{X_C}{R} = 0.577$$

$$\frac{X_C}{8} = 0.577$$

$$X_C = 4.618 \Omega$$

$$\frac{1}{\omega C} = 4.618$$

$$\omega = \frac{1}{4.618 \times 30 \times 10^{-6}} = 7218.13$$

$$2\pi f = 7218.13$$

$$f = \frac{7218.13}{2\pi} = 1149 \text{ Hz}$$

8. An RC series circuit with $R = 10 \Omega$ an impedance with an angle -45° at a frequency $f_1 = 500 \text{ Hz}$. Find the frequency for which the absolute value of the impedance is twice that of f_1 .

Solution: Since the impedance angle is negative, the series circuit is RC and phase angle

$$\phi = \tan^{-1} \left(\frac{-X_C}{R} \right)$$

$$-45^\circ = \tan^{-1} \left(\frac{-X_C}{10} \right)$$

$$\frac{-X_C}{10} = \tan(-45^\circ)$$

$$X_C = 10$$

$$C = \frac{1}{2\pi f_C \times 10} = 31.83 \mu\text{F}$$

The impedance value is

$$Z = R - jX_C = 10 - j10 = 14.14 \angle -45^\circ$$

If the absolute value of impedance is doubled, then

$$\cos(-\phi) = \frac{R}{Z} = \frac{10}{28.28} = 0.3536$$

$$\phi = -69.29^\circ$$

$$-X_C = R \tan \phi = -26.46$$

$$\frac{1}{2\pi f_2 C} = 26.46$$

$$f_2 = \frac{1}{2 \times \pi \times 26.46 \times 31.83 \times 10^{-6}} = 198 \text{ Hz}$$

9. A voltmeter placed across the 3Ω resistor shown in figure reads 45. What is the ammeter reading.

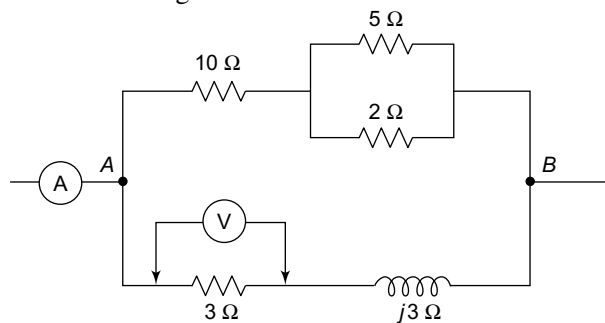


Fig. 5.9

Solution: The current through 3- Ω resistor

$$I = (3) = 45 \text{ V}$$

$$I_1 = 15 \text{ amp.}$$

The voltage across each branch $V_{AB} = 15 (3 + j3)$

$$= 63.63 \angle 45^\circ$$

Since same voltage is applied to another branch, the current I_2 is

$$\begin{aligned} I_2 &= \frac{V_{AB}}{Z_{eq}} = \frac{63.63 \angle 45^\circ}{[10 + (5//2)]} \\ &= \frac{63.63 \angle 45^\circ}{11.428} = 5.567 \angle 45^\circ \text{ amp} \end{aligned}$$

Total current

$$\begin{aligned} I_T &= I_1 + I_2 \\ &= 15 + 5.567 \angle 45^\circ = 19.34 \angle 11.74^\circ \text{ amp} \end{aligned}$$

The ammeter reading is 19.34 amp.

10. In the circuit shown in the figure at a frequency $\omega = 400 \text{ rad/s}$ the current leads the voltage by 63.4° . Find R and the voltage across each circuit element. Draw the voltage phasor diagram.

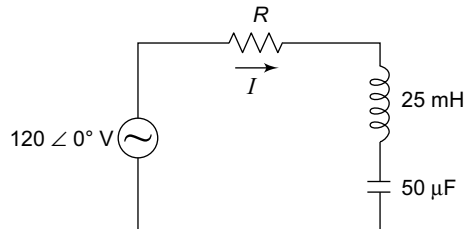


Fig. 5.10

Solution: Inductive reactance $X_L = \omega L = 400 \times 25 \times 10^{-3} = 10 \Omega$

$$\text{Capacitive reactance } X_C = \frac{1}{\omega C} = \frac{1}{400 \times 50 \times 10^{-6}} = 50 \Omega$$

Total impedance

$$\begin{aligned} Z &= R + j(X_L - X_C) \\ &= R + j(10 - 50) \\ &= (R - j40) \Omega \end{aligned}$$

Since the current leads the voltage by 63.4°

$$Z \angle \theta = \sqrt{R^2 + (40)^2} \left[\tan^{-1} \left(\frac{-40}{R} \right) \right]$$

$$Z \angle -63.4^\circ = \sqrt{R^2 + (40)^2} \left[\tan^{-1} \left(\frac{-40}{R} \right) \right]$$

$$\tan^{-1} \left(\frac{-40}{R} \right) = -63.4^\circ$$

$$R = \frac{-40}{\tan(-63.4^\circ)} = 20 \, \Omega$$

Total impedance is

$$Z = 20 - j40 = 44.7 \angle -63.4^\circ \, \Omega$$

Current in the circuit is

$$I = \frac{V}{Z} = \frac{120 \angle 0^\circ}{44.7 \angle -63.4^\circ} = 2.68 \angle 63.4^\circ \text{ amp.}$$

Voltage across resistor $V_R = IR = 20 \times 2.68 \angle 63.4^\circ$

$$= 53.6 \angle 63.4^\circ$$

Voltage across inductive reactance

$$V_L = IX_L = 2.68 \angle 63.4^\circ \times 10 \angle +90^\circ$$

$$= 26.8 \angle 153.4^\circ$$

Voltage across capacitive reactance

$$V_C = IX_C = 2.68 \angle 63.4^\circ \times 50 \angle -90^\circ$$

$$= 134 \angle -26.6^\circ \text{ V}$$

The phasor diagram is

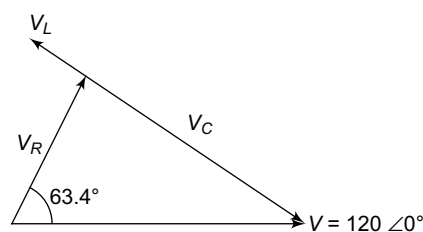


Fig. 5.11

Objective-Type Questions

1. A voltage 5 V, 10 kHz applied to a capacitance of $0.005\ \mu\text{F}$, then the value of current is
 - (a) 1.57 mA
 - (b) 3.18 A
 - (c) 1.57 A
 - (d) 5 A
2. Capacitive reactance is _____ proportional to frequency and capacitance.
 - (a) directly
 - (b) inversely
 - (c) equal to
 - (d) none of the above
3. A voltage 5 V, 10 kHz applied to an inductance of 100 mH, then the current flowing through it is
 - (a) 5 amp
 - (b) 10 amp
 - (c) $795.8\ \mu\text{A}$
 - (d) $795.8\ \mu\text{A}$
4. At what frequency is the reactance of $50\ \mu\text{H}$ inductor equal to $800\ \Omega$?
 - (a) 255 kHz
 - (b) 2.55 kHz
 - (c) 25.5 MHz
 - (d) 2.55 MHz
5. What is the phase angle between the capacitor current and applied voltage in a parallel RC circuit?
 - (a) 90°
 - (b) 0°
 - (c) 45°
 - (d) 25°
6. In a certain parallel RC circuit, the resistor current is 10 mA, and the capacitor current is 15 mA. Determine the phase angle and total current.
 - (a) 50° , 8 mA
 - (b) 56.3° , 18 mA
 - (c) 90° , 18 mA
 - (d) 45° , 8 mA
7. When the frequency of the applied voltage in a series RL circuit is increased, what happens to the phase angle?
 - (a) Increases
 - (b) Decreases
 - (c) Remains same
 - (d) Zero