

Steady State AC Analysis

- Using nodal analysis, determine the node voltage V_2 in the network given below.

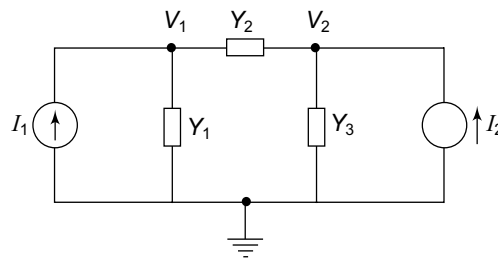


Fig. 7.1

$$I_1 = 10 \angle 0^\circ \text{ A}; I_2 = 10 \angle 60^\circ \text{ A}; Y_1 = (0.5 - j1.0) \text{ S}$$

$$Y_2 = (0.2 - j0.6) \text{ S}; Y_3 = (0.8 - j0.6) \text{ S}$$

Solution: To obtain the voltage V_1 , applying KCL at node 1 considering the branch currents

$$I_1 = V_1 Y_1 + (V_1 - V_2) Y_2$$

$$V_1 (Y_1 + Y_2) - V_2 Y_2 = I_1 \quad (1)$$

To obtain the voltage V_2 , applying KCL at node 2 considering the branch currents

$$I_2 = (V_2 - V_1) Y_2 + V_2 Y_3$$

$$-V_1 Y_2 + V_2 (Y_2 + Y_3) = I_2 \quad (2)$$

From the given data, the equations (1) and (2) becomes

$$V_1 (0.5 - j1.0) + 0.2 - j0.6 - V_2 (0.2 - j0.6) = 10 \angle 0^\circ$$

$$-V_1 (0.2 - j0.6) + V_2 (0.2 - j0.6 + 0.8 - j0.6) = 10 \angle 60^\circ$$

By simplifying, we get

$$(0.7 - j1.6) V_1 - (0.2 - j0.6) V_2 = 10 \angle 0^\circ$$

$$-(0.2 - j0.6) V_1 + (1 - j1.2) V_2 = 10 \angle 60^\circ$$

By using Cramers' rule

$$\begin{bmatrix} (0.7 - j1.6) & -(0.2 - j0.6) \\ -(0.2 - j0.6) & (1 - j1.2) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \angle 0^\circ \\ 10 \angle 60^\circ \end{bmatrix}$$

$$\Delta = \begin{vmatrix} (0.7 - j1.6) & -(0.2 - j0.6) \\ -(0.2 - j0.6) & (1 - j1.2) \end{vmatrix} = -0.9 - j2.2$$

$$\Delta_2 = \begin{vmatrix} (0.7 - j1.6) & 10 \angle 0^\circ \\ -(0.2 - j0.6) & 10 \angle 60^\circ \end{vmatrix} = 19.356 - j7.938$$

$$V_2 = \frac{19.356 - j7.938}{-(0.9 + j2.2)} = 8.8 \angle 89.951^\circ$$

2. For the given network, find current through $(2 + j3) \Omega$ impedance using mesh analysis.

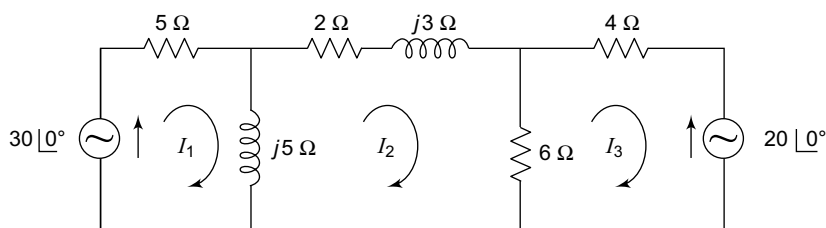


Fig. 7.2

Solution: Applying KVL to loop 1, 2 and 3

$$(5 + j5)I_1 - j5I_2 = 30 \angle 0^\circ$$

$$-j5I_1 + (8 + j8)I_2 - 6I_3 = 0$$

$$-6I_2 + 10I_3 = -20 \angle 0^\circ \text{ V}$$

$$\begin{bmatrix} 5 + j5 & -j5 & 0 \\ -j5 & 8 + j8 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 30 \angle 0^\circ \\ 0 \\ -20 \angle 0^\circ \end{bmatrix}$$

To obtain current in $(2 + j3) \Omega$ impedance

$$I_2 = \frac{\Delta_2}{\Delta}$$

where
$$\Delta_2 = \begin{bmatrix} 5 + j5 & 30\angle 0^\circ & 0 \\ -j5 & 0 & -6 \\ 0 & -22\angle 0^\circ & 10 \end{bmatrix}$$

and
$$\Delta = \begin{bmatrix} 5 + j5 & -j5 & 0 \\ -j5 & 8 + j8 & -6 \\ 0 & -6 & 10 \end{bmatrix} = 70 + j60$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{(5 + j5)(-120\angle 0^\circ) - 30\angle 0^\circ(-j50)}{70 + j60}$$

$$\therefore I_2 = 1.74 \angle 40.1^\circ \text{ A}$$

3. For the given network, determine the voltage of nodes 1 and 2 with respect to the selected reference.

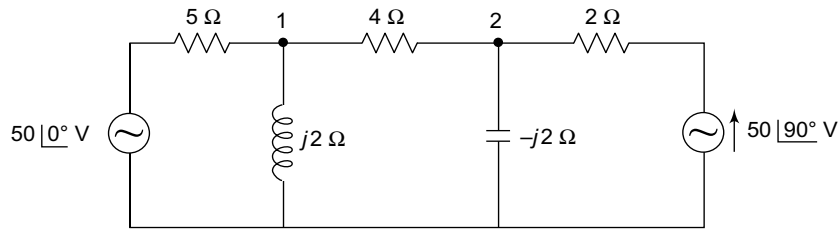


Fig. 7.3

Solution: Applying KCL at nodes 1 and 2 to determine voltage V_1 and V_2 .

$$\frac{V_1 - 50\angle 0^\circ}{5} + \frac{V_1}{j2} + \frac{V_1 - V_2}{4} = 0$$

$$\frac{V_2 - V_1}{4} + \frac{V_2}{-j2} + \frac{V_2 - 50\angle 90^\circ}{2} = 0$$

$$V_1 \left[\frac{1}{5} + \frac{1}{j2} + \frac{1}{4} \right] - \frac{V_2}{4} = \frac{50\angle 0^\circ}{5} \quad (1)$$

$$-\frac{V_1}{4} + V_2 \left[\frac{1}{4} - \frac{1}{j2} + \frac{1}{2} \right] = \frac{50\angle 90^\circ}{2} \quad (2)$$

The above equations are written in matrix form

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \begin{bmatrix} \left(\frac{1}{5} + \frac{1}{j2} + \frac{1}{4}\right) & \left(\frac{-1}{4}\right) \\ \left(\frac{-1}{4}\right) & \left(\frac{1}{4} - \frac{1}{j2} + \frac{1}{2}\right) \end{bmatrix} = \begin{bmatrix} 10 \angle 0^\circ \\ 25 \angle 90^\circ \end{bmatrix}$$

$$V_1 = \frac{\begin{vmatrix} 10 \angle 0^\circ & -\frac{1}{4} \\ 25 \angle 90^\circ & \left(\frac{1}{4} - \frac{1}{j2} + \frac{1}{2}\right) \end{vmatrix}}{\begin{vmatrix} \left(\frac{1}{5} + \frac{1}{j2} + \frac{1}{4}\right) & \left(\frac{-1}{4}\right) \\ \left(\frac{-1}{4}\right) & \left(\frac{1}{4} - \frac{1}{j2} + \frac{1}{2}\right) \end{vmatrix}} = 24.7 \angle 72.25^\circ \text{ V}$$

$$V_2 = \frac{\begin{vmatrix} \left(\frac{1}{5} + \frac{1}{j2} + \frac{1}{4}\right) & 10 \angle 0^\circ \\ \left(\frac{-1}{4}\right) & 25 \angle 90^\circ \end{vmatrix}}{\begin{vmatrix} \left(\frac{1}{5} + \frac{1}{j2} + \frac{1}{4}\right) & \left(\frac{-1}{4}\right) \\ \left(\frac{-1}{4}\right) & \left(\frac{1}{4} - \frac{1}{j2} + \frac{1}{2}\right) \end{vmatrix}} = 33.6 \angle 53.75^\circ \text{ V}$$

4. Apply the superposition theorem to the network given below and find current I .

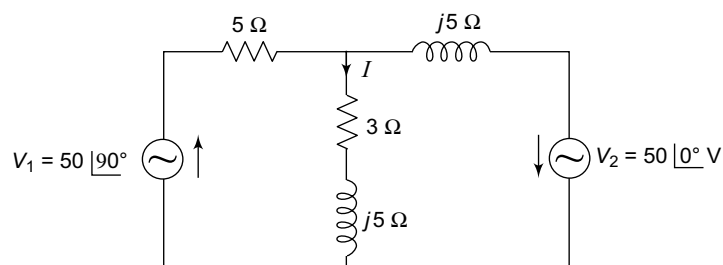


Fig. 4

Solution: According to the superposition theorem, the current due to the $50 \angle 90^\circ$ voltage source is I' , with voltage source $50 \angle 0^\circ$ V short circuited.

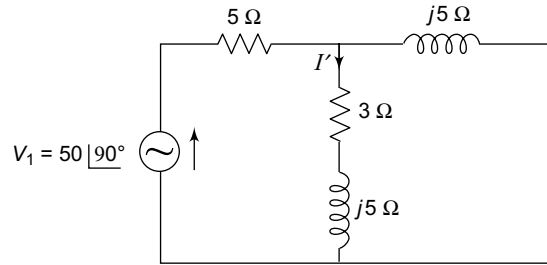


Fig. 5

Total impedance of the circuit is

$$Z_T = \frac{(3 + j5)(j5)}{3 + j10} = 6.3 \angle 25.4^\circ \Omega$$

Total current in the circuit

$$I_T = \frac{V_1}{Z_T} = \frac{50 \angle 90^\circ}{6.3 \angle 25.4^\circ} = 7.93 \angle 64.6^\circ \text{ A}$$

The current in $(3 + j5) \Omega$ due to V_1 is

$$I' = \frac{(7.93 \angle 64.6^\circ)(j5)}{3 + j10} = 3.8 \angle 81.3^\circ \text{ A}$$

The current due to $50 \angle 0^\circ$ V voltage source is I'' , with voltage source $50 \angle 90^\circ$ V being shorted.

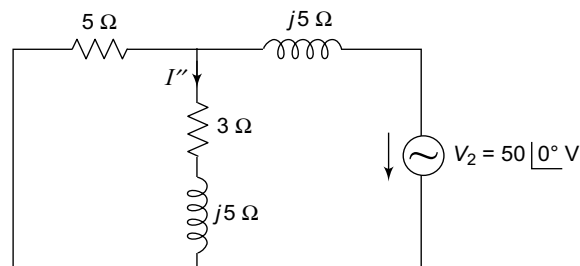


Fig. 6

The total impedance of the circuit at terminals V_2 is

$$Z_T = j5 + \frac{5(3 + j5)}{8 + j5} = \frac{-25 + j40 + 15 + j25}{8 + j5}$$

$$Z_T = 6.97 \angle 66.74^\circ \Omega$$

The total current delivered by V_2 is

$$I_T = \frac{V_2}{Z_T} \times \frac{50 \angle 0^\circ}{6.97 \angle 66.74^\circ} = 7.17 \angle -66.74^\circ \text{ A}$$

Therefore, the current

$$I'' = -I_T \times \frac{5}{8 + j5} = -7.17 \angle -66.74^\circ \times \frac{5}{8 + j5}$$

$$I'' = 3.8 \angle -98.74^\circ \text{ A}$$

The current in $(3 + j5) \Omega$ impedance due to two sources $I = I' + I''$

$$= 3.8 \angle 81.3^\circ + 3.8 \angle -98.74^\circ$$

$$I = 0$$

5. In the circuit shown in the given figure. Find the value of R_L which results in maximum power transfer. Calculate the value of the maximum power.

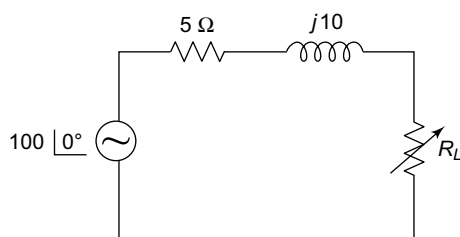


Fig. 7.7

Solution: The value of R_L for which the maximum power transfer

$$R_L = |5 + j10| = \sqrt{5^2 + 10^2} = 11.18 \Omega$$

Then the current in the circuit is

$$I = \frac{100 \angle 0^\circ}{11.18 + 5 + j10} = \frac{100 \angle 0^\circ}{19.02 \angle 31.718^\circ}$$

$$I = 5.26 \angle -31.718^\circ$$

The maximum power across RL is

$$P_{\max} = I^2 R = (5.26)^2 11.18 = 309 \text{ watts.}$$

6. Obtain the Thevenin equivalent circuit at terminals AB shown in the figure.

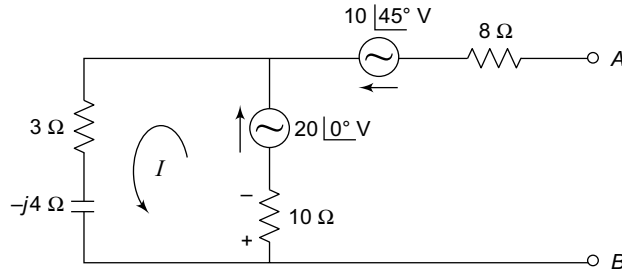


Fig. 7.8

Solution: When terminals AB are open circuited, the current is

$$I = \frac{20 \angle 0^\circ}{10 + 3 - j4} = 1.47 \angle 17.1^\circ \text{ A}$$

The voltage drop across the 10Ω resistor

$$V_{10} = I(10) = 14.7 \angle 17.1^\circ \text{ V}$$

$$V_{Th} = V_{AB} = 20 \angle 0^\circ - 10 \angle 45^\circ - 14.7 \angle 17.1^\circ$$

$$V_{Th} = 11.39 \angle 264.4^\circ \text{ V}$$

The impedance

$$Z' = 8 + \frac{10(3 - j4)}{10 + 3 - j4} = 10.97 - j2.16 \Omega$$

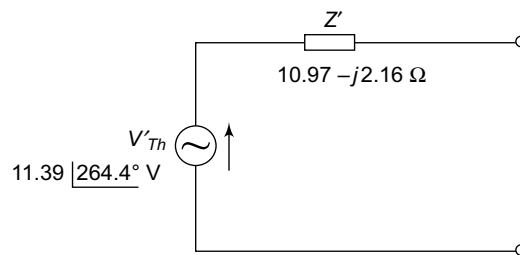


Fig. 7.9

7. Find the Norton equivalent circuit for the circuit shown in the figure.

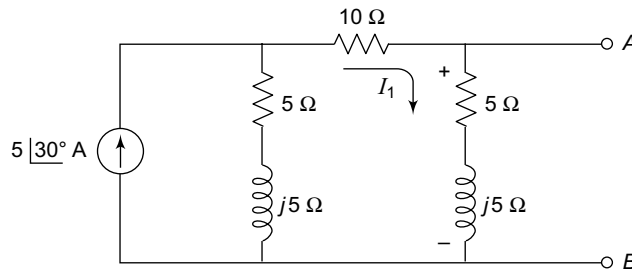


Fig. 7.10

Solution: The equivalent impedance Z_{eq} at terminals AB

$$Z_N = Z_{eq} = \frac{(5 + j5)(15 + j5)}{(5 + j5 + 15 + j5)} = 4 + j3 \, \Omega$$

$$= 5 \angle 36.9^\circ \, \Omega$$

when AB terminals are short circuited.

The current through short circuit is

$$I_N = 5 \angle 30^\circ \times \frac{5 + j5}{15 + j5} = 2.24 \angle 56.6^\circ \, \text{A}$$

The Norton equivalent circuit is

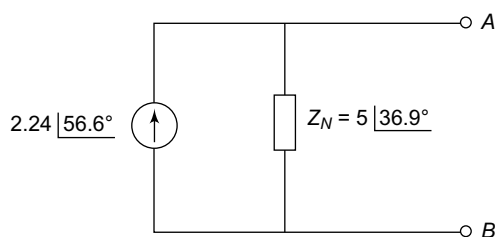


Fig. 11

8. By application of the Thevenin's theorem, find the current I in the circuit shown in the figure. The voltage source shown is sinusoidal having a 10 V rms value and the frequency is such that the inductor has an impedance of magnitude $20 \, \Omega$ and each capacitor has an impedance of magnitude $10 \, \Omega$.

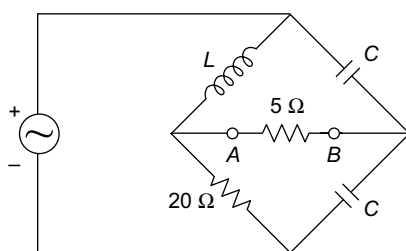


Fig. 12

Solution: The impedance of the circuit at terminals AB when voltage source is short circuited.

$$Z_{AB} = \frac{20 \times 20}{20 + 20} + \frac{10 \times 10}{10 + 10} = 15 \, \Omega$$

The Thevenin's equivalent voltage

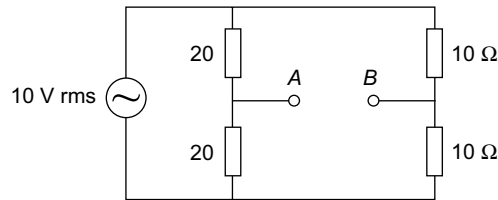


Fig. 7.13

$$V_{AB} = 10 \times \frac{20}{40} = 5 \text{ V}$$

The Thevenin's equivalent circuit is

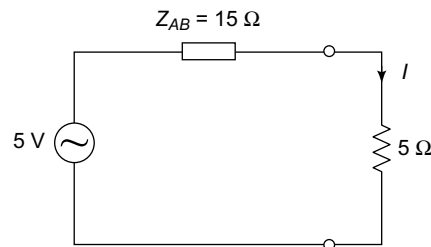


Fig. 7.14

The current I flowing through 5Ω resistor will be

$$I = \frac{5}{15 + 5} = \frac{5}{20} = 0.25 \text{ A}$$

9. In the circuit shown in the figure, the resistance R_g is variable between 2 and 55 ohms. What value of R_g results in maximum power transfer across terminals AB ?

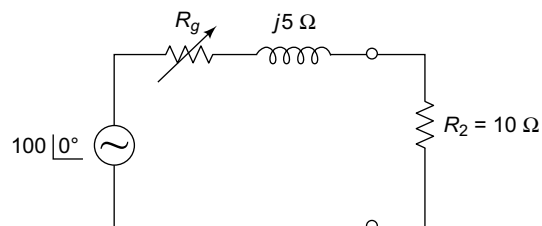


Fig. 7.15

Solution: In the given circuit load R_2 is fixed. Thus the maximum power transfer do not apply. However, the current result when R_g is minimum. Minimum given value of R_g is 2 ohm.

Then

$$Z_T = 2 + j5 + 10 = (12 + j5) \Omega$$

Therefore
$$I_{\max} = \frac{V}{Z_T} = \frac{100 \angle 0^\circ}{12 + j5} = 7.7 \angle -22.6^\circ$$

$$\begin{aligned}\text{Maximum power} &= I_{\max}^2 R \\ &= (7.7)^2 \times 10 = 593 \text{ watts.}\end{aligned}$$

Objective-Type Questions

1. One of the following theorems makes use of equivalent voltage generator in circuit analysis.
 - (a) Norton's theorem
 - (b) Maximum power transfer theorem
 - (c) Thevenin's theorem
 - (d) Superposition theorem
2. Conditions of maximum power transfer apply to
 - (a) current source alone
 - (b) voltage source alone
 - (c) both current and voltage sources
 - (d) none of the above
3. Superposition theorem applies to
 - (a) d.c. circuits only
 - (b) a.c. circuits only
 - (c) a.c. and d.c. with voltage sources
 - (d) a.c. and d.c. with voltage and current sources or mixed-type sources
4. During analysis of Thevenin's theorem, we have to consider
 - (a) Power dissipated only in the load
 - (b) Power dissipated only in the generator