

Chapter 13

Application of the Laplace Transform in Circuit Analysis

1. Find the Laplace transform of the signal $t(0.5)^t u(t)$.

Solution: $f(t) = t(0.5)^t u(t)$

$$\begin{aligned}\text{Consider } L[(0.5)^t] &= \int_0^{\infty} (0.5)^t e^{-St} dt \\ &= \int_0^{\infty} (0.5 e^{-S})^t dt\end{aligned}$$

Let $0.5 e^{-S} = x$

$$\int_0^{\infty} (x)^t dt = \left[\frac{xt}{\log x} \right]_0^{\infty} = \frac{x^{\infty}}{\log x} - \frac{1}{\log x}$$

Since $x = 0.5 e^{-S}$

$$L[(0.5)^t] = \frac{-1}{\log 0.5 e^{-S}}$$

If $f(t) \xrightarrow{L} F(S)$, then $t.f(t) \xrightarrow{L} \frac{-d}{dS} F(S)$

$$\begin{aligned}\therefore L[t(0.5)^t] &= \frac{-d}{dS} \left[\frac{-1}{\log (0.5 e^{-S})} \right] \\ &= \frac{d}{dS} \left[\frac{1}{\log (0.5 e^{-S})} \right]\end{aligned}$$

$$\frac{d}{dS} \left[\frac{1}{\log(0.5 e^{-S})} \right] = \frac{\frac{1}{0.5 e^{-S}} e^{-S} (-1)}{\left(\log(0.5 e^{-S}) \right)^2}$$

$$\therefore L[t(0.5)^t u(t)] = \frac{-e^{-S}}{(-0.5 e^{-S}) \left[\log(0.5 e^{-S}) \right]^2}$$

2. Find the Laplace transform of the waveform $x(t)$ shown in the figure.

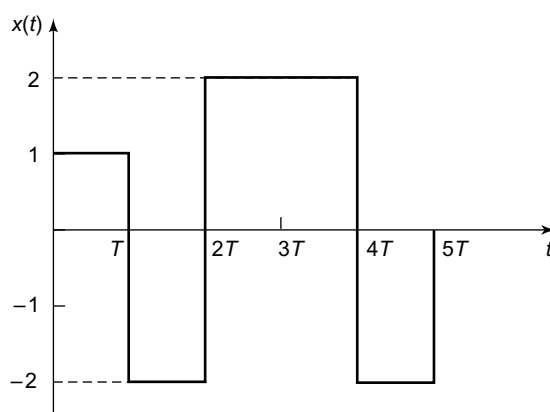


Fig. 13.1

Solution: By definition,

$$\begin{aligned} L[x(t)] &= \int_0^{\infty} e^{-St} x(t) dt \\ &= \int_0^T e^{-St} dt - \int_T^{2T} 2e^{-St} dt + \int_{2T}^{4T} 2e^{-St} dt - \int_{4T}^{5T} 2e^{-St} dt \\ &= \left[\frac{-1}{S} e^{-St} \right]_0^T - \left[\frac{-2}{S} e^{-St} \right]_T^{2T} + \left[\frac{-2}{S} e^{-St} \right]_{2T}^{4T} - \left[\frac{-2}{S} e^{-St} \right]_{4T}^{5T} \\ &= \left[\frac{1}{S} - \frac{1}{S} e^{-ST} \right] + \left[\frac{2}{S} e^{-2ST} - \frac{2}{S} e^{-ST} \right] - \left[\frac{2}{S} e^{-4ST} - \frac{2}{S} e^{-2ST} \right] \\ &\quad + \left[\frac{2}{S} e^{-5ST} - \frac{2}{S} e^{-4ST} \right] \\ X(S) &= \frac{1}{S} [1 - 3e^{-ST} + 4e^{-2ST} - 4e^{-4ST} + 2e^{-5ST}] \end{aligned}$$

3. Find the signal $y(t)$, the Laplace transform of which is

$$Y(S) = \frac{S^3 + 7S^2 + 18S + 20}{S^2 + 5S + 6}$$

Solution: The fraction can be written as

$$Y(S) = 3 + 2 + \frac{2S + 8}{S^2 + 5S + 6}$$

Taking partial fraction for $\frac{2S + 8}{S^2 + 5S + 6}$, we get

$$\frac{2S + 8}{S^2 + 5S + 6} = \frac{A}{S + 3} + \frac{B}{S + 2}$$

$$A = \left. \frac{2S + 8}{(S + 3)(S + 2)} (S + 3) \right|_{S = -3} = -2$$

$$B = \left. \frac{2S + 8}{(S + 3)(S + 2)} (S + 2) \right|_{S = -2} = 4$$

$$Y(S) = S + 2 - \frac{2}{S + 3} + \frac{4}{S + 2}$$

Taking inverse transform both sides, we get

$$y(t) = \frac{d}{dt} S(t) + 2 \cdot \delta(t) - 2e^{-3t} u(t) + 4e^{-2t} u(t)$$

4. State and explain the initial value theorem of a Laplace transform. Using the initial value theorem, find the initial value of the signal corresponding to the Laplace transform

$$Y(S) = \frac{S + 1}{S(S + 2)}$$

Verify that the answer obtained is correct.

Solution: Refer section 13.4.

Initial value theorem states that

$$\lim_{t \rightarrow 0} f(t) = \lim_{S \rightarrow \infty} SF(S)$$

Consider $\lim_{S \rightarrow \infty} SY(S) = \lim_{S \rightarrow \infty} \frac{S + 1}{S + 2} = \frac{1 + 1/S}{1 + 2/S}$

$$\therefore \lim_{S \rightarrow \infty} SY(S) = 1$$

By taking inverse Laplace transform of $Y(S)$, we get $y(t)$

$$Y(S) = \frac{S+1}{S(S+2)} = \frac{A}{S} + \frac{B}{S+2}$$

$$A = SY(S)\big|_{S=0} = \frac{S+1}{S+2}\bigg|_{S=0} = \frac{1}{2}$$

$$B = (S+2)Y(S)\big|_{S=-2} = \frac{S+1}{S}\bigg|_{S=-2} = \frac{1}{2}$$

$$Y(S) = \frac{1}{2S} + \frac{1}{2(S+2)}$$

Taking inverse transform of both sides, we get

$$y(t) = \frac{1}{2} u(t) + \frac{1}{2} e^{-2t} u(t)$$

$$y(t)\big|_{t=0} = \frac{1}{2} + \frac{1}{2} = 1$$

Hence, the initial value theorem is verified.

5. Find the inverse Laplace transform of

$$F(S) = \frac{1}{(S+2)^2}$$

Solution: The function can be written as

$$F(S) = F_1(S), F_2(S) = \frac{1}{S+2} \cdot \frac{1}{S+2}$$

We can use the convolution integral here:

$$f_1(t) = e^{-2t} u(t)$$

$$f_2(t) = e^{-2t} u(t)$$

By using convolution property, we have

$$f(t) = \int_0^t f_1(\tau) f_2(t-\tau) d\tau$$

$$= \int_0^t e^{-2\tau} \cdot e^{-2(t-\tau)} d\tau$$

$$= e^{-2t} \int_0^t d\tau$$

$$= e^{-2t} [\tau]_0^t$$

$$f(t) = te^{-2t} u(t)$$

6. For the circuit given, determine, the current in resistor 10Ω when the switch is closed at $t = 0$, using Laplace transforms. Assume initial current through inductor is zero.

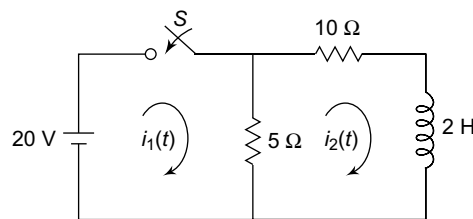


Fig. 13.2

Solution: When the switch is closed at $t = 0$, applying KVL in the circuit

$$5 [i_1(t) - i_2(t)] = 20 \quad (1)$$

$$5 [i_2(t) - i_1(t)] + 10i_2(t) + 2 \frac{di_2(t)}{dt} = 0 \quad (2)$$

Taking Laplace transform for the above equation

$$5I_1(S) - 5I_2(S) = \frac{20}{S} \quad (3)$$

$$-5I_1(S) + 15I_2(S) + 2S I_2(S) = 0 \quad (4)$$

Add (3) and (4)

$$I_2(S) [10 + 2S] = \frac{20}{S}$$

$$I_2(S) = \frac{20}{S (2S + 10)}$$

$$I_2(S) = \frac{10}{S (S + 10)} = \frac{A}{S} + \frac{B}{S + 5}$$

$$A = \frac{10}{S(S+5)} S \Big|_{S=0} = 2$$

$$B = \frac{10}{S(S+5)} (S+5) \Big|_{S=5} = -2$$

$$\therefore I_2(S) = \frac{2}{S} - \frac{2}{S+5}$$

Taking inverse Laplace transform on both sides, we get

$$i_2(t) = 2u(t) - 2e^{-5t} u(t)$$

Therefore, the current through $10\ \Omega$ resistor is

$$i_2(t) = 2(1 - e^{-5t}) u(t) \text{ amp.}$$

7. The network shown in the figure is initially under steady-state condition with the switch in the position 1. The switch is moved from the position 1 to the position 2 at $t \neq 0$. Calculate the current $i(t)$ through R_1 after switching.

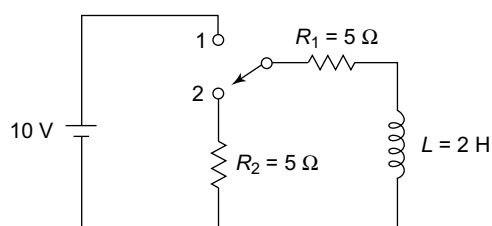


Fig. 13.3

Solution: When the switch is at the position 1, the steady-state current in the inductor

$$i = \frac{10}{5} = 2 \text{ A}$$

when the switch is at the position 2

$$Ri(t) + L \frac{di(t)}{dt} = 0$$

Taking Laplace transforms on both sides

$$RI(S) + L [SI(S) - i(0)] = 0$$

$$(R + SL) I(S) = Li(0)$$

$$(10 + 2S) I(S) = 2 \times 2$$

$$I(S) = \frac{2}{S + 5}$$

Taking inverse transform on both sides, we get

$$i(t) = 2e^{-5t}$$

8. In the network shown in the figure, the switch is closed at $t = 0$ and there is no initial charge on either of the capacitors. Find the current i by the Laplace transform method.

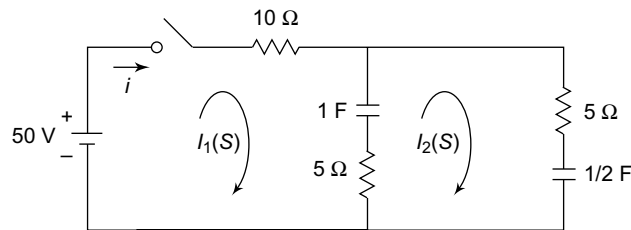


Fig. 13.4

Solution: Taking network transform, we have

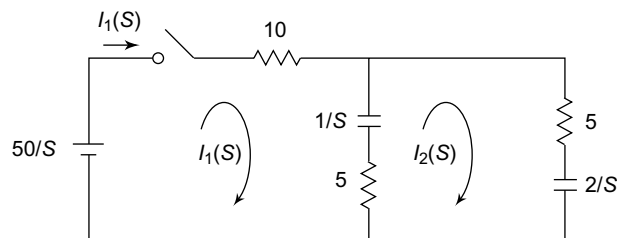


Fig. 13.5

On applying KVL to both loops, we get

$$\frac{50}{S} = 15I_1(S) - 5I_2(S) + \frac{I_1(S)}{S} - \frac{I_2(S)}{S} \quad (1)$$

$$0 = I_1(S) \left[-5 + \frac{1}{S} \right] + I_2(S) \left[10 + \frac{3}{S} \right] \quad (2)$$

From equation (2)

$$I_2(S) = \frac{\left(-5 + \frac{1}{S} \right)}{10 + \frac{3}{S}} I_1(S) \quad (3)$$

On substituting equation (3) in equation (1), we get

$$I_1(S) = \frac{500S + 150}{-2 + 35S + 125S^2}$$

$$I_1(S) = \frac{4(S + 0.25)}{(S + 0.328)(S - 0.04)} = \frac{A}{S + 0.328} + \frac{B}{S - 0.04}$$

From the above equation

$$A = \frac{4(S + 0.25)}{(S + 0.328)(S - 0.04)} (S + 0.328) \Big|_{S = -0.328}$$

$$A = 1.179$$

$$B = \frac{4(S + 0.25)}{(S + 0.328)(S - 0.04)} (S - 0.04) \Big|_{S = 0.04}$$

$$B = 3.15$$

$$I(S) = I_1(S) = \frac{1.179}{S + 0.328} + \frac{3.15}{S - 0.04}$$

By taking inverse Laplace transform

$$i(t) = 1.1179e^{-0.328t} + 3.15e^{+0.04t}$$

9. A sinusoidal voltage of $12 \sin 8t$ volts is applied at $t = 0$ to a series circuit of $R = 4 \Omega$ and $L = 1$ H. By Laplace transform method, determine the circuit current $i(t)$ for all $t \geq 0$. Assume zero initial conditions.

Solution:

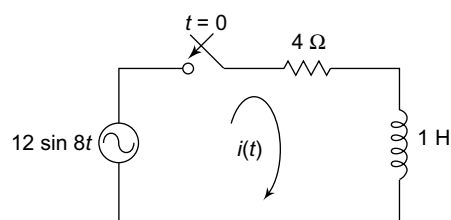


Fig. 13.6

Applying KVL in the circuit, for $t \geq 0$

$$12 \sin 8t = 4i(t) = L \frac{di(t)}{dt}$$

Taking Laplace transforms on both sides

$$\frac{12.8}{s^2 + 8^2} = 4I(s) + sI(s)$$

$$(\because i(0) = 0)$$

$$I(s) = \frac{96}{(s^2 + 8^2)(s + 4)}$$

Taking partial fractions

$$I(s) = \frac{As + B}{s^2 + 8^2} + \frac{C}{s + 4}$$

$$I(s) = \frac{-1.2s + 4.8}{s^2 + 8^2} + \frac{1.2}{s + 4}$$

$$I(s) = -1.2 \frac{s}{s^2 + 8^2} + \frac{4.8}{8} \frac{8}{s^2 + 8^2} + \frac{1.2}{s + 4}$$

Taking inverse transforms on both sides, we get

$$i(t) = (-1.2 \cos 8t + 0.6 \sin 8t + 1.2 e^{-4t}) \text{ amp.}$$

10. Consider the circuit shown in the figure, the switch is thrown from position 1 to 2 at time $t = 0$. Just before the switch is thrown, the initial conditions are $i_L(0+) = 2\text{A}$, $v_C(0+) = 2\text{V}$. Find the current $i(t)$ after the switch is thrown.

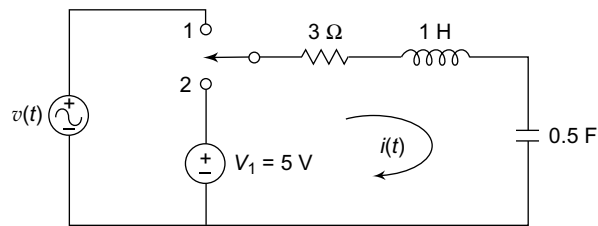


Fig. 13.7

Solution: At $t > 0$, the current $i(t)$ can be obtained by using KVL.

The loop equation is

$$3i(t) + 1 \frac{di(t)}{dt} + \frac{1}{0.5} \int i(t) dt = 5V$$

Taking Laplace transforms on both sides

$$3I(s) + 1 [sI(s) - i(0+)] + \frac{1}{0.5} \left[\frac{I(s)}{s} \right] + \left[\frac{v_C(0+)}{s} \right] = \frac{5}{s}$$

$$3I(S) + SI(S) - 2 + \frac{2}{S} I(S) + \frac{5}{S} = \frac{5}{S}$$

$$\left(3 + S + \frac{2}{S}\right) I(S) = \frac{5}{S} + 2 - \frac{2}{S}$$

$$\frac{3S + S^2 + 2}{S} I(S) = \frac{3 + 2S}{S}$$

$$I(S) = \frac{2S + 3}{S^2 + 3S + 2} = \frac{A}{S + 1} + \frac{B}{S + 2}$$

$$A = \frac{2S + 3}{(S + 1)(S + 2)} (S + 1) \Big|_{S = -1} = 1$$

$$B = \frac{2S + 3}{(S + 1)(S + 2)} (S + 2) \Big|_{S = -2} = 1$$

$$I(S) = \frac{1}{S + 1} + \frac{1}{S + 2}$$

Taking inverse Laplace transforms on both sides

$$i(t) = e^{-t} u(t) + e^{-2t} u(t)$$

Objective-Type Questions

- The Laplace transformation of $f(t)$ is $F(S)$. Given $F(S) = \frac{\omega}{S^2 + \omega^2}$, the final value of $f(t)$ is
 - infinity
 - zero
 - one
 - none of the above
- The Laplace transform of the function $i(t)$ is

$$I(S) = \frac{10S + 4}{S(S + 1)(S^2 + 4S + 5)}, \text{ its final value will be}$$

- | | |
|-------------------|-------------------|
| (a) $\frac{4}{5}$ | (b) $\frac{5}{4}$ |
| (c) 4 | (d) 5 |

3. If $L[f(t)] = \frac{2(S+1)}{S^2+2S+5}$, then $f(0+)$ and $f(\infty)$ are given by
- 0, 2 respectively
 - 2, 0 respectively
 - 0, 1 respectively
 - $\frac{2}{5}$, 0 respectively
4. The Laplace transform of the waveform shown in the figure will be

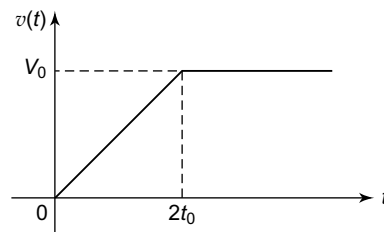


Fig. 13.8

- $\frac{V_o}{t_o S^2} [1 - e^{-t_o S}] - \frac{V_o}{S} e^{-2t_o S}$
 - $\frac{V_o}{t_o S^2} [1 - e^{-t_o S} + e^{-2t_o S}]$
 - $\frac{V_o}{S} - \frac{V_o}{t_o S^2} (e^{-2t_o S} + e^{-3t_o S})$
 - $\frac{V_o}{t_o S^2} (e^{-t_o S}) - \frac{V_o}{S} e^{-t_o S}$
5. Laplace transform of the function e^{-20t} is
- $\frac{1}{S-20}$
 - $S+20$
 - $S-20$
 - $\frac{1}{S+20}$

6. The inverse transform of $\frac{2}{S+3}$ is

- (a) $2(t+3)$
- (b) $2e^{-3t}$
- (c) e^{-3t}
- (d) $2e^{-t}$

7. Laplace transform of damped sine wave $e^{-3t} \sin 50t$ is

- (a) $\frac{1}{(S+3)^2 + 50^2}$
- (b) $\frac{S}{(S+3)^2 + 50^2}$
- (c) $\frac{50}{(S+3)^2 + 50^2}$
- (d) $\frac{50^2}{(S+3)^2 + 50^2}$