

Chapter 15

Two-Port Networks

1. Determine the Z-parameters for the circuit shown in the figure.

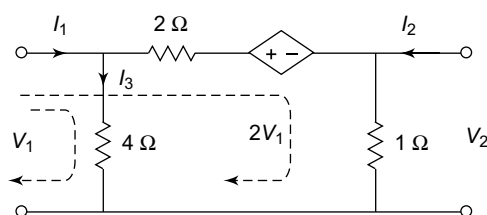


Fig. 15.1

Solution: Let I_3 be the current in $4\ \Omega$

$$V_1 = 4 I_3 \Rightarrow I_3 = \frac{V_1}{4}$$

$$V_2 = 2(I_1 - I_3) + I_2 \Rightarrow V_2 = 2 I_1 - \frac{V_1}{2} + I_2$$

Applying KVL to outer loop

$$u I_3 - (I_1 - I_3 + I_2) - 2 V_1 - 2(I_1 - I_3) = 0$$

$$2 V_1 = -3 I_1 - I_2 + 6 I_3$$

$$2 V_1 = -3 I_1 - I_2 + \frac{V_1}{2}$$

$$\frac{V_1}{2} = -3 I_1 - I_2$$

$$V_1 = -6 I_1 - 2 I_2 \quad (1)$$

Substituting in V_2

$$\begin{aligned} V_2 &= 2I_1 + I_2 - (-3I_1 - I_2) \\ V_2 &= 5I_1 - 2I_2 \end{aligned} \quad (2)$$

From equations (1) and (2)

$$\begin{aligned} Z_{11} &= -6; & Z_{12} &= -2 \\ Z_{21} &= 5; & Z_{22} &= -2 \end{aligned}$$

2. For the current shown in problem 1, find Y -parameters.

Solution: Subtracting Equation (1) from (2)

$$V_1 - V_2 = -6I_1 - 2I_2 - 5I_1 + 2I_2$$

$$I_1 = \frac{-V_1}{11} + \frac{V_2}{11} \quad (3)$$

In order to eliminate I_1 ; multiply equation 2 with $\frac{6}{5}$ and add it to equation 1

$$\begin{aligned} V_2 \times \frac{6}{5} &= 6I_1 - \frac{12}{5}I_2 \\ V_1 &= -6I_1 - 2I_2 \\ V_1 + \frac{6}{5}V_2 &= \frac{-22}{5}I_2 \\ I_2 &= -\frac{5}{22}V_1 - \frac{3}{11}V_2 \end{aligned} \quad (4)$$

From equations (3) and (4)

$$\begin{aligned} Y_{11} &= \frac{-1}{11}; & Y_{12} &= \frac{1}{11} \\ Y_{21} &= \frac{-5}{22}; & Y_{22} &= \frac{-3}{11} \end{aligned}$$

3. For the Two-port network shown in the figure, the input impedance with cd open = $125 + j50$. Input impedance with cd short = $200 + j150$; output impedance with ab open = 100Ω . Find Z_A ; Z_B and Z_C .

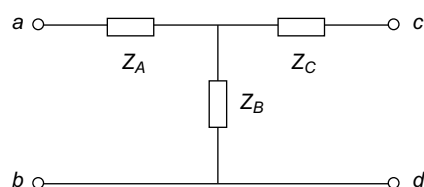


Fig. 15.2

Solution: From the given data

$$Z_{11} = 125 + j50$$

$$Z_{22} = 100$$

$$\frac{1}{Y_{11}} = 200 + j150$$

The following relations hold good for a T network

$$Z_A = Z_{11} - Z_{12}$$

$$Z_B = Z_{21} - Z_{12}$$

$$Z_C = Z_{22} - Z_{12}$$

Also
$$Y_{11} = \frac{Z_{22}}{4Z} = \frac{Z_{22}}{Z_{11} Z_{22} - Z_{12} Z_{21}}$$

$$\therefore Z_{11} Z_{22} - Z_{12} Z_{21} = (100) (200 + j150)$$

$$Z_{12} = Z_{21}$$

$$\begin{aligned} \therefore Z_{12}^2 &= -100 (200 + j150) + Z_{11} Z_{22} \\ &= -100 (200 + j150) + 100 (125 + j50) \end{aligned}$$

$$Z_{12}^2 = 12500 \angle 233.13^\circ$$

$$Z_{12} = 111.8 \angle 116.565^\circ = -50 + j100$$

$$\therefore Z_A = 125 + j100 + 50 - j100 = 175 - j50$$

$$Z_B = Z_{12} = -50 + j100$$

$$Z_C = 100 + 50 - j100 = 150 - j100.$$

4. Find the transmission parameters for the network shown in the figure.

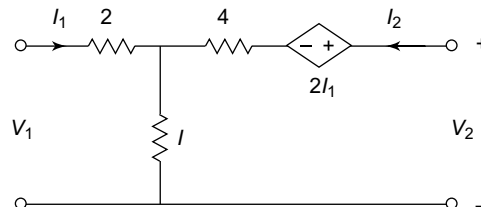


Fig. 15.3

$$\text{Solution: } V_1 = AV_2 - BI_2; \quad A = \left. \frac{V_1}{V_2} \right|_{I_2=0}; \quad -B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$I_1 = CV_2 - DI_2, \quad C = \left. \frac{I_1}{V_2} \right|_{I_2=0}; \quad -D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

$$\text{when } I_2 = 0; \quad V_1 = 3I_1$$

$$\text{and } -V_2 + 2I_1 + I_1 = 0$$

$$4V_2 + 3I_1 = 0$$

$$V_2 = 3I_1 \Rightarrow \frac{I_1}{V_2} = \frac{1}{3} = C$$

$$V_1 = 3I_1$$

$$V_1 = 3 \frac{V_2}{3} \Rightarrow \frac{V_1}{V_2} = 1 = A$$

When $V_2 = 0$; the network is as shown in the figure.

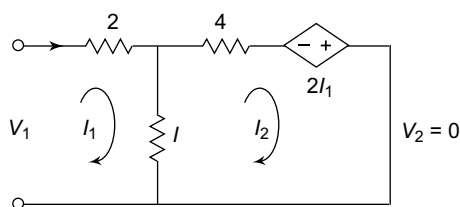


Fig. 15.4

Loop equation for the 1st loop

$$V_1 = 3I_1 - I_2$$

Loop equation for the 2nd loop

$$-2I_1 + I_2 - I_1 + 4I_2 = 0$$

$$3I_1 = 5I_2 \Rightarrow \frac{I_1}{I_2} = \frac{5}{3} = -D$$

$$V_1 = 3 \times \frac{5}{3} I_2 - I_2 = 4I_2$$

$$\frac{V_1}{I_2} = 4 = -B$$

5. For the parallel networks shown in the figure obtain the Y -parameters of the combination.

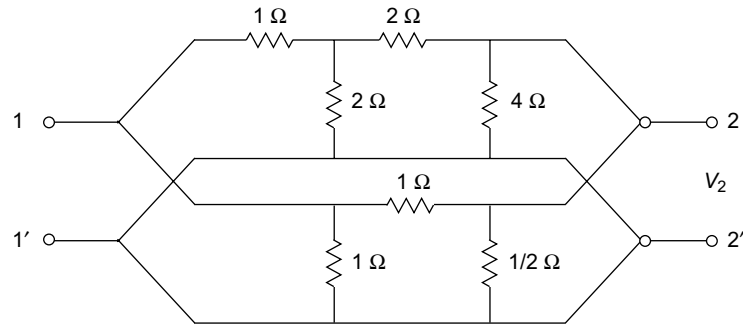


Fig. 15.5

Solution: The Y -parameters of the upper network are given

$$Y_{11} = \frac{1}{2} \text{ } \mathfrak{U}; \quad Y_{21} = \frac{-1}{4} \text{ } \mathfrak{U};$$

$$Y_{22} = \frac{5}{8} \text{ } \mathfrak{U} \text{ and } Y_{12} = \frac{-1}{4} \text{ } \mathfrak{U}$$

The Y -parameters of the lower network are given by

$$Y_{11} = 2; \quad Y_{12} = -1;$$

$$Y_{22} = 3 \text{ and } Y_{21} = -1$$

Y -parameters of the combination are given by

$$Y_{11} = \frac{1}{2} + 2; \quad Y_{12} = \frac{-1}{4} - 1$$

$$Y_{21} = \frac{-1}{4} - 1; \quad Y_{22} = \frac{5}{8} + 3$$

6. If the Y -parameters of a network are given by $Y_{11} = \frac{1}{2}$; $Y_{12} = Y_{21} = 1$ and $Y_{22} = \frac{1}{2}$. Find inverse transmission parameters

Solution:

$$\Delta Y = \begin{vmatrix} \frac{1}{2} & 1 \\ 1 & \frac{1}{2} \end{vmatrix} = \frac{-3}{4}$$

$$A^1 = \frac{-Y_{11}}{Y_{12}} = \frac{1}{2}; \quad B^1 = \frac{-1}{Y_{12}} = -1$$

$$C^1 = \frac{-\Delta Y}{Y_{12}} = \frac{3}{4}; \quad D^1 = \frac{-Y_{22}}{Y_{12}} = \frac{-1}{2}$$

7. Obtain the Z-parameters for the two-port unsymmetrical lattice network shown in the figure.

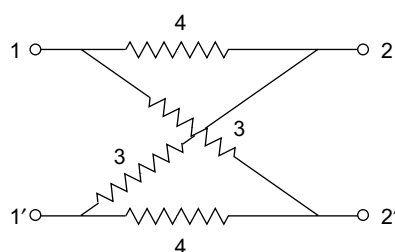


Fig. 15.6

Solution:

$$Z_{11} = \frac{(Z_a + Z_b)(Z_d + Z_c)}{Z_a + Z_b + Z_c + Z_d}$$

where Z_a, Z_d are called series impedances and Z_b, Z_c are called the diagonal of the network.

Since the network is symmetrical

$$Z_{11} = \frac{Z_a + Z_b}{2} = \frac{7}{2} = Z_{22}$$

$$Z_{12} = Z_{21} = \frac{Z_b - Z_a}{2} = \frac{3 - 4}{2} = \frac{-1}{2}$$

8. For the network shown in the figure, obtain Z-parameters, h-parameters and inverse h-parameters.

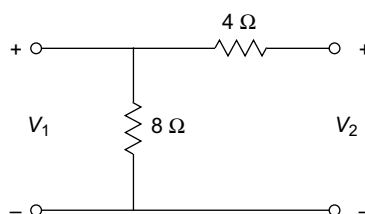


Fig. 15.7

Solution: The Z-parameters can be directly written from the figure.

$$Z_{11} = 8 \, \Omega; \quad Z_{12} = Z_{21} = 8 \, \Omega; \quad Z_{22} = 12 \, \Omega$$

h -parameters can be expressed in terms of Z-parameters as

$$h_{11} = \frac{\Delta Z}{Z_{22}} \quad \text{where } \Delta Z = \begin{vmatrix} 8 & 8 \\ 8 & 12 \end{vmatrix} = 32$$

$$\therefore h_{11} = \frac{32}{12} = \frac{8}{3}; \quad h_{12} = \frac{Z_{12}}{Z_{22}} = \frac{8}{12} = \frac{2}{3}$$

$$h_{21} = \frac{-Z_{21}}{Z_{22}} = \frac{-8}{12} = \frac{-2}{3}; \quad h_{22} = \frac{1}{Z_{22}} = \frac{1}{12}$$

$$g_{11} = \frac{1}{Z_{11}} = \frac{1}{8} \, \text{S}; \quad g_{12} = \frac{-Z_{12}}{Z_{11}} = -1$$

$$g_{21} = \frac{Z_{21}}{Z_{11}} = 1; \quad g_{22} = \frac{\Delta Z}{Z_{11}} = 8$$

Objective-Type Questions

- A Two-port network
 - is always an active network
 - is always a passive network
 - both active or passive
- A Two-port network without sources are called
 - active parts
 - passive parts
 - linear parts
- A Two-port network with sources in their branches are called
 - active parts
 - passive parts
 - non-linear parts
- The Two-port network is reciprocal of
 - the determinant of the Transmission matrix = 1
 - $Z_{12} = Z_{21}$
 - both a and b
- For a Two-port bilateral network
 - $AD - BC = 0$
 - $AD - BC = -1$
 - $AD - BC = 1$
- The Z-parameters of a symmetrical T network are $Z_{11} = 3 \, \Omega$; $Z_{12} = Z_{21} = 2$; $Z_{22} = 3 \, \Omega$, then the series and diagonal elements of an equivalent lattice are
 - $3 \, \Omega$; $2 \, \Omega$
 - $2 \, \Omega$; $3 \, \Omega$
 - $1 \, \Omega$; $5 \, \Omega$

7. The h -parameters for the current shown in the figure are given by

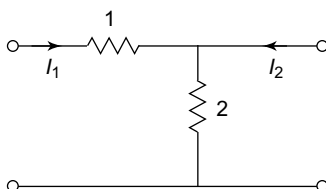


Fig. 15.8

- (a) $\begin{bmatrix} 1 & 1 \\ -1 & \frac{1}{2} \end{bmatrix}$ (b) $\begin{bmatrix} 1 & -1 \\ 1 & \frac{1}{2} \end{bmatrix}$ (c) $\begin{bmatrix} 1 & \frac{1}{2} \\ -1 & 1 \end{bmatrix}$
8. The Z -parameters of the network given in question number 7 are
 (a) $\begin{bmatrix} 2 & 2 \\ 2 & 3 \end{bmatrix}$ (b) $\begin{bmatrix} 2 & 3 \\ 2 & 2 \end{bmatrix}$ (c) $\begin{bmatrix} 3 & 2 \\ 2 & 2 \end{bmatrix}$
9. Dimensionally the units of h_{11} represents
 (a) admittance (b) impedance (c) voltage gain
10. Dimensionally the units of h_{12} represent
 (a) open circuit output admittance
 (b) short circuit input impedance
 (c) open circuit reverse voltage gain