

---

# Contents

*Preface*

*xi*

<b>1. PN Junction Diode</b>	<b>1.1–1.52</b>
1.1 Introduction	1.1
1.2 Classification of Semiconductors	1.1
1.2.1 Intrinsic Semiconductor	1.1
1.2.2 Extrinsic Semiconductor	1.2
1.3 Qualitative Theory of PN Junction Diode	1.4
1.3.1 PN Junction Diode in Equilibrium with no Applied Voltage	1.4
1.3.2 Operation and Volt–Ampere Characteristics of a Diode Under Forward Bias Condition	1.9
1.3.3 Operation and Volt–Ampere Characteristics of a Diode Under Reverse Bias Condition	1.10
1.3.4 Limiting Values of PN Junction Diode	1.11
1.4 PN Junction as a Diode	1.11
1.5 Energy Band Structure of Open Circuited PN Junction	1.12
1.6 Diode Equation	1.15
1.7 Ideal Versus Practical—Resistance Levels (Static and Dynamic)	1.21
1.8 Transition or Space Charge (or Depletion Region) Capacitance ( $C_T$ )	1.26
1.8.1 Step-graded Junction	1.27
1.9 Diffusion (or Storage) Capacitance ( $C_d$ )	1.29
1.10 Temperature Dependence of V–I Characteristics of Diodes	1.31
1.10.1 Effect of Temperature on Reverse Saturation Current	1.33
1.10.2 Temperature Dependence of V–I Characteristics	1.34
1.11 Diode Equivalent Circuits	1.36
1.11.1 Load Line Analysis	1.37
1.12 Piecewise Linear Diode Model/Diode Equivalent Circuits	1.39
1.13 Breakdown Mechanisms in Semi Conductor Diodes	1.40
1.14 PN Diode Applications	1.42
1.15 Zener Diode Characteristics	1.42
1.15.1 Avalanche Breakdown	1.43
1.15.2 Zener Breakdown	1.43
1.15.3 Effect of Temperature on Zener Diode	1.43
1.15.4 Applications	1.44
1.16 Specifications of Semiconductor Diodes	1.45
<i>Review Questions</i>	1.45
<i>Objective Type Questions</i>	1.46
<i>Answers</i>	1.51

<b>2. Rectifiers And Filters</b>	<b>2.1–2.57</b>
2.1 Introduction	2.1
2.2 Linear Mode Power Supply	2.2
2.2.1 Requirements of Linear Mode Power Supply	2.2
2.3 P–N Junction Diode as a Rectifier	2.3
2.4 Rectifiers	2.3
2.4.1 Half-wave Rectifier	2.3
2.4.2 Full-wave Rectifier	2.12
2.4.3 Bridge Rectifier	2.19
2.5 Harmonic Components in a Rectifier Circuit	2.23
2.6 Filters	2.24
2.6.1 Inductor Filter	2.24
2.6.2 Capacitor Filter	2.26
2.6.3 L-Section or LC Filter	2.29
2.6.4 CLC or $\pi$ -section Filter	2.33
2.6.5 R–C Filters	2.34
2.6.6 Comparison of Filters	2.35
2.7 Voltage Regulation Using Zener Diode	2.35
2.7.1 Zener Diode Shunt Regulator	2.36
2.7.2 Emitter-follower Type Regulator	2.43
2.7.3 Principle of Obtaining a Regulated Power Supply	2.44
2.7.4 Principle of Obtaining a Dual Tracking Voltage Regulator	2.46
2.7.5 Transistorised Shunt Regulator	2.47
2.7.6 Transistorised Series Regulator	2.47
2.7.7 Adjustable Voltage Regulators	2.50
<i>Review Questions</i>	2.52
<i>Objective Type Questions</i>	2.54
<i>Answers</i>	2.57
<b>3. Bipolar Junction Transistor</b>	<b>3.1–3.34</b>
3.1 Introduction	3.1
3.2 Construction of BJT And BJT Symbols	3.1
3.3 Transistor Biasing	3.2
3.4 BJT Operation and Transistor Current Components	3.2
3.4.1 Operation and Current Components of NPN Transistor	3.2
3.4.2 Operation and Current Components of PNP Transistor	3.3
3.5 Types of Transistor Amplifier Configuration	3.6
3.5.1 Common Base Configuration	3.6
3.5.2 Common Emitter Configuration	3.9
3.5.3 Common Collector Configuration	3.12
3.5.4 Comparison	3.13
3.5.5 Current Amplification Factor	3.13
3.6 Transistor as an Amplifier	3.14
3.7 Large Signal, DC, And Small Signal CE Values of Current Gain	3.15
3.8 Limits of Operation (Breakdown in Transistors)	3.16
3.8.1 Avalanche Breakdown and Multiplication	3.16

3.8.2	Reach-through or Punch-through	3.17
3.9	BJT Specifications	3.29
	<i>Review Questions</i>	3.29
	<i>Objective Type Questions</i>	3.30
	<i>Answers</i>	3.34
<b>4.</b>	<b>Transistor Biasing and Stabilization</b>	<b>4.1–4.48</b>
4.1	Introduction	4.1
4.2	Bias Stability	4.1
4.2.1	Operating Point, Need for Biasing and Bias Stabilization Against Variations in $V_{BE}$ and $\beta$	4.1
4.2.2	DC Load Line	4.2
4.2.3	AC Load Line	4.3
4.2.4	Stability Factor (S)	4.7
4.3	Methods of Transistor Biasing	4.8
4.3.1	Fixed Bias or Base Resistor Method	4.8
4.3.2	Emitter-feedback Bias	4.12
4.3.3	Collector-to-Base Bias or Collector-Feedback Bias	4.14
4.3.4	Collector–Emitter Feedback Bias	4.18
4.3.5	Voltage Divider Bias, Self Bias, or Emitter Bias	4.19
4.4	Stabilization Factors	4.20
4.4.1	Common Base Stability	4.37
4.4.2	Advantage of Self Bias (Voltage Divider Bias) Over Other Types of Biasing	4.38
4.5	Bias Compensation Using Diode And Transistor	4.38
4.5.1	Diode Compensation	4.38
4.5.2	Thermistor Compensation	4.38
4.5.3	Sensistor Compensation	4.39
4.6	Thermal Runaway	4.39
4.7	Thermal Resistance	4.40
4.8	Condition for Thermal Stability	4.41
4.9	Types of Heat Sinks	4.43
	<i>Review Questions</i>	4.44
	<i>Objective Type Questions</i>	4.46
	<i>Answers</i>	4.48
<b>5.</b>	<b>Field Effect Transistor</b>	<b>5.1–5.26</b>
5.1	Introduction	5.1
5.2	Construction of <i>N</i> -Channel JFET	5.1
5.3	Principle of Operation, Pinch-off Voltage, Volt–Ampere Characteristics and Symbols of JFET	5.2
5.4	Characteristic Parameters of the JFET	5.4
5.5	Expression for Saturation Drain Current	5.9
5.6	Slope of the Transfer Characteristic at $IDSS$	5.10
5.7	The JFET Small-signal Model	5.12
5.8	Applications of JFET	5.14
5.9	Metal Oxide Semiconductor Field Effect Transistor (MOSFET)	5.14

5.10	Construction, Principle of Operation and Symbols of Enhancement MOSFET	5.15
5.11	Construction, Principle of Operation and Symbols of Depletion MOSFET	5.16
5.12	Comparison of MOSFET with JFET	5.17
5.13	Handling Precautions for MOSFET	5.18
5.14	Comparison of <i>N</i> -with <i>P</i> -Channel MOSFETS	5.19
5.15	Comparison of <i>N</i> -with <i>P</i> -Channel FETS	5.20
5.16	Applications of MOSFET in CMOS Circuits	5.20
5.16.1	Digital	5.20
5.16.2	Analog	5.21
5.17	Advantages of BJT over MOSFET	5.22
5.18	Specifications of JFET and MOSFET	5.22
	<i>Review Questions</i>	5.22
	<i>Objective Type Questions</i>	5.24
	<i>Answers</i>	5.26
<b>6.</b>	<b>FET Amplifiers</b>	<b>6.1–6.46</b>
6.1	Introduction	6.1
6.2	Common Source (CS) Amplifier	6.1
6.3	Common Drain (CD) Amplifier	6.5
6.4	Common Gate (CG) Amplifier	6.7
6.5	A Generalized FET Amplifier	6.10
6.5.1	Output from the Drain	6.10
6.5.2	For CS Amplifier	6.11
6.5.3	For CG Amplifier	6.11
6.5.4	Output from the Source	6.12
6.5.5	For CD Amplifier	6.12
6.6	Biasing the FET	6.13
6.6.1	Fixing the Q-point	6.13
6.6.2	Self-bias	6.15
6.6.3	Voltage Divider Bias	6.15
6.6.4	Fixed Bias	6.16
6.7	Biasing the MOSFET	6.17
6.7.1	Biasing of Enhancement MOSFET	6.17
6.7.2	Biasing of Depletion MOSFET	6.18
6.8	The FET Model at High Frequency	6.30
6.8.1	The Common Source (CS) Amplifier at High Frequencies	6.31
6.8.2	The Common-drain Amplifier at High Frequencies	6.34
6.9	Frequency Response of FET Amplifier	6.35
6.10	Comparison of JFET and BJT	6.36
6.11	FET as Voltage-variable Resistor (VVR)	6.37
6.12	UJT (Unijunction Transistor)	6.37
6.13	Specifications of MOSFET and UJT	6.42
	<i>Review Questions</i>	6.42
	<i>Objective Type Questions</i>	6.43
	<i>Answers</i>	6.45

<b>7. Small Signal Low Frequency BJT Models</b>	<b>7.1–7.66</b>
7.1 Introduction	7.1
7.2 Two-port Devices and Network Parameters	7.1
7.2.1 Z-Parameters or Impedance Parameters	7.2
7.2.2 Y-Parameters or Admittance Parameters	7.2
7.2.3 Hybrid Parameters or $h$ -Parameters	7.3
7.2.4 Notations used in Transistor Circuits	7.4
7.3 The Hybrid Model for two-port Network	7.4
7.3.1 Determination of $h$ -Parameters from Transistor Characteristics	7.4
7.4 Analysis of a Transistor Amplifier Circuit using $h$ -Parameters	7.7
7.4.1 Current Gain or Current Amplification, $A_i$	7.8
7.4.2 Input Impedance, $Z_i$	7.8
7.4.3 Voltage Gain or Voltage Amplification Factor, $A_V$	7.9
7.4.4 Output Admittance, $Y_O$	7.10
7.4.5 Voltage Amplification ( $A_{VS}$ ) Taking into Account the Resistance ( $R_S$ ) of the Source	7.10
7.4.6 Current Amplification ( $A_{IS}$ ) Taking into Account the Source Resistance ( $R_S$ )	7.11
7.4.7 Operating Power Gain, $A_p$	7.12
7.4.8 Comparison of CB, CE and CC Transistor Amplifier Configurations	7.13
7.5 Simplified CE Hybrid Model	7.14
7.5.1 Generalised Approximate Model	7.16
7.5.2 Common Emitter Amplifier with Emitter Resistor	7.20
7.6 Analysis of CC Amplifier using the Approximate Model	7.23
7.7 Analysis of CB Amplifier using the Approximate Model	7.26
7.8 Low Frequency Response of Transistor Amplifier	7.28
7.8.1 Effect of Emitter Bypass Capacitor (CE) on Low Frequency Response	7.28
7.9 Effect of Coupling Capacitor CC on Low Frequency Response	7.33
7.10 Single Stage Amplifiers	7.34
7.10.1 Common Emitter Amplifier	7.34
7.10.2 Common Collector (CC) Amplifier	7.36
7.10.3 Common Base (CB) Amplifier	7.38
7.11 Small Signal Analysis of Single Stage BJT Amplifiers	7.39
7.11.1 CE Amplifier with Fixed Bias	7.39
7.11.2 CE Amplifier with Unbypassed Emitter Resistor	7.43
7.11.3 CE Amplifier with Voltage-divider Bias	7.48
7.11.4 CB Amplifier	7.50
7.11.5 CC Amplifier (or) Emitter Follower	7.52
<i>Review Questions</i>	7.63
<i>Objective Type Questions</i>	7.64
<i>Answers</i>	7.66

<b>8. Special Purpose Electronic Devices</b>	<b>8.1–8.24</b>
8.1 Introduction	8.1
8.2 Principle of Operation and Characteristics of Tunnel Diode	8.1
8.3 Principle of Operation and Characteristics of Varactor Diode	8.4
8.4 Principle of Operation of Schottky Barrier Diode	8.5
8.5 Principle of Operation of Silicon Controlled Rectifier (SCR)	8.6
8.5.1 PNP Diode (Shockley Diode)	8.6
8.5.2 SCR (Silicon Controlled Rectifier)	8.7
8.5.3 Thyristor Ratings	8.9
8.5.4 Rectifier Circuits Using SCR	8.10
8.5.5 LASCR (Light Activated SCR)	8.14
8.6 Principle of Operation of Semiconductor Photodiode	8.14
8.7 Specifications of Special Purpose Electronic Devices	8.15
<i>Review Questions</i>	8.16
<i>Objective Type Questions</i>	8.17
<i>Answers</i>	8.19
<i>Appendix A Specifications of Semiconductor Devices</i>	<i>A1–A11</i>
<i>Appendix B Probable Value of General Physical Constants</i>	<i>B1</i>
<i>Appendix C Conversion Factors and Prefixes</i>	<i>C1</i>
<i>Solved Question Papers 2010</i>	
Set 1 .....	QP1.1-1.17
Set 2 .....	QP1.18-1.32
Set 3 .....	QP1.33-1.49
Set 4 .....	QP1.50-1.72
<i>Solved Question Papers 2011</i>	
Set 1 .....	QP1.73-1.77
Set 2 .....	QP1.78-1.82
Set 3 .....	QP1.83-1.89
Set 4 .....	QP1.90-1.94