

Solutions

10.1

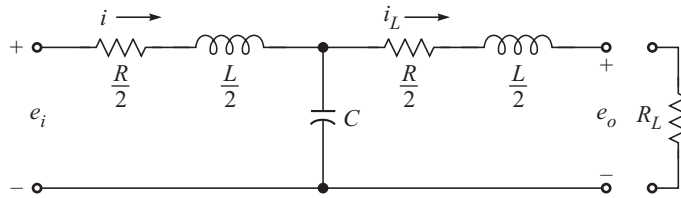


Fig. 1

Output of the cable is connected to a load R_L . Applying Kirchhoff's voltage law to both the loops, the first loop satisfies

$$\frac{R}{2}i + \frac{L}{2}Di + \frac{1}{CD}(i - i_L) = e_i \quad (1)$$

Multiplying by CD throughout, Eq. (1) becomes

$$\frac{RCD}{2}i + \frac{LCD^2}{2}i + i - i_L = e_i CD \quad (2)$$

The second loop satisfies the following equation

$$\left(\frac{R}{2} + R_L\right)i_L + \frac{L}{2}Di_L + \frac{1}{CD}(i_L - i) = 0 \quad (3)$$

Multiplying Eq. (3) throughout by CD

$$CD\left(\frac{R}{2} + R_L\right)i_L + \frac{LCD^2}{2}i_L + i_L - i = 0 \quad (4)$$

Assembling Eqs. (2) and (4) into a matrix

$$\begin{Bmatrix} i \\ i_L \end{Bmatrix} = \begin{bmatrix} \frac{RCD}{2} + \frac{LCD^2}{2} + 1 & -1 \\ -1 & \left(\frac{R}{2} + R_L\right)CD + \frac{LCD^2}{2} + 1 \end{bmatrix}^{-1} \begin{Bmatrix} e_i CD \\ 0 \end{Bmatrix} \quad (5)$$

$$\begin{Bmatrix} i \\ i_L \end{Bmatrix} = \frac{1}{\det} \begin{bmatrix} \left(\frac{R}{2} + R_L\right)CD + \frac{LCD^2}{2} + 1 & 1 \\ 1 & \frac{RCD}{2} + \frac{LCD^2}{2} + 1 \end{bmatrix} \begin{Bmatrix} e_i CD \\ 0 \end{Bmatrix} \quad (6)$$

$$\begin{aligned} \det = CD & \left[\frac{RCD}{2} \left(\frac{R}{2} + R_L \right) + \frac{RLCD^2}{4} + \frac{R}{2} + \frac{LCD^2}{2} \left(\frac{R}{2} + R_L \right) \right. \\ & \left. + \frac{L^2 CD^3}{4} + \frac{L}{2} D + \left(\frac{R}{2} + R_L \right) + \frac{LD}{2} \right] \end{aligned} \quad (7)$$

$$\det = CD (R + R_L) \left\{ \frac{D^3 L^2 C}{4(R + R_L)} + \frac{D^2 LC}{2} + \frac{D}{(R + R_L)} \left[\frac{RC}{2} \left(\frac{R}{2} + R_L \right) + L \right] + 1 \right\} \quad (8)$$

$$i_L = \frac{e_i CD}{\det} \quad (9)$$

$$e_0 = i_L R_L \quad (10)$$

From Eqs. (8), (9) and (10)

$$\frac{e_0}{e_i}(D) = \frac{\frac{R_L}{(R + R_L)}}{\frac{D^3 L^2 C}{4(R + R_L)} + \frac{D^2 LC}{2} + \frac{D}{(R + R_L)} \left[\frac{RC}{2} \left(\frac{R}{2} + R_L \right) + L \right] + 1} \quad (11)$$

$$R = 20 \, \Omega, \quad C = 0.3 \, \mu\text{F}, \quad L = 0.2 \, \text{mH}$$

$$\text{Let } R_L = 1 \, \text{M}\Omega$$

using the above values in Eq. (11)

$$\frac{e_0}{e_i}(D) = \frac{0.999}{2.99 \times 10^{-21} D^3 + 3 \times 10^{-11} D^2 + 3 \times 10^{-6} D + 1} \quad (12)$$

For $R_L = \infty$, Eq. (12) becomes

$$\frac{e_0}{e_i}(D) = \frac{1}{3 \times 10^{-11} D^2 + 3 \times 10^{-6} D + 1} \quad (13)$$

The Bode plot of Eq. (13) is shown in Fig. 2.

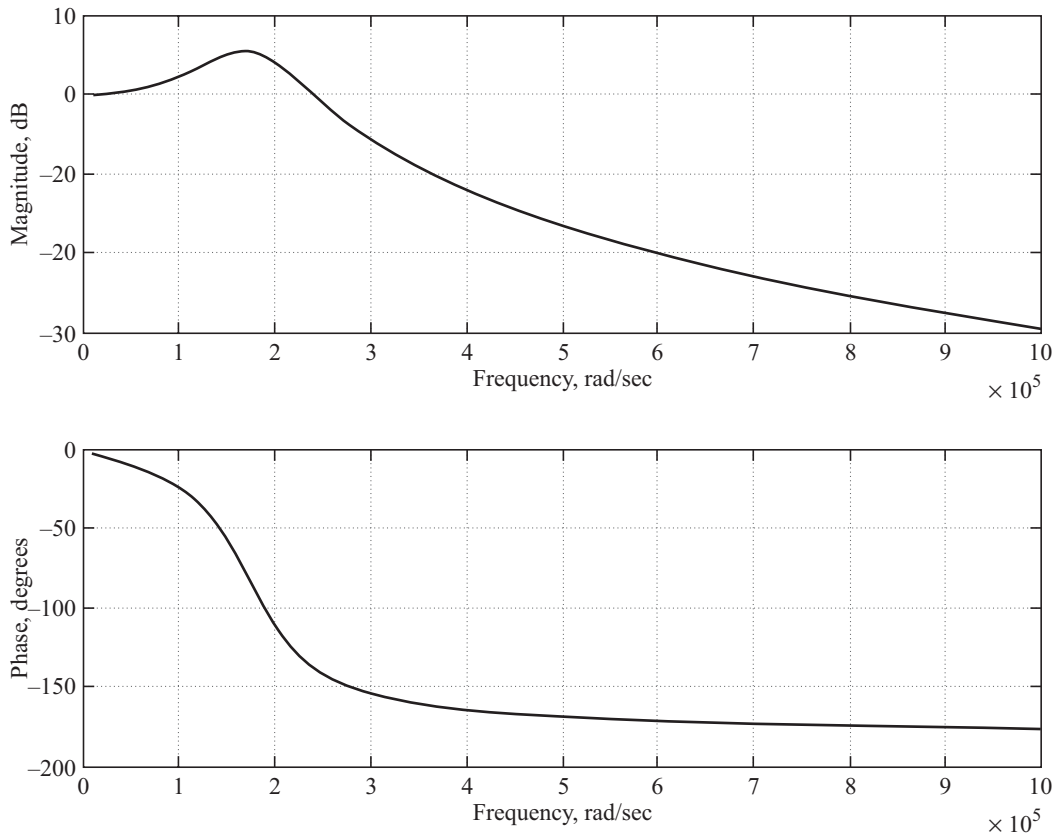


Fig. 2

10.2 Synchro repeater system

Number of transmitters	1
Number of receivers	5
Torque gradient of a single pair, for short cable	0.0035 N-m/deg
Percentage of torque gradient lost due to cable resistance	10% per ohm
Friction of each receiver	0.00035 N-m/deg
Cable resistance	0.16667 Ω /m
$L_{\max} = ?$	

Torque gradient, when all the devices are connected

$$\begin{aligned}
 &= \frac{0.0035 \times 2}{5 + 1} \\
 &= 1.16667 \times 10^{-3} \text{ N-m/deg}
 \end{aligned}$$

Total torque gradient lost due to cable resistance

$$\begin{aligned}
 &= 2 \times 0.0035 \times 0.1 \\
 &= 7 \times 10^{-4} \text{ N-m/deg}/\Omega \\
 &= 7 \times 10^{-4} \times 0.16667 L_{\max} \frac{\text{N-m}}{\text{deg}} \\
 &= 1.16667 \times 10^{-4} L_{\max}
 \end{aligned}$$

Total torque gradient between devices

– torque gradient lost due to cable resistance = friction

$$\begin{aligned}
 1.16667 \times 10^{-3} - 1.16667 \times 10^{-4} L_{\max} &= 0.00035 \\
 L_{\max} &= 7 \text{ m (between each pair)}
 \end{aligned}$$

10.3

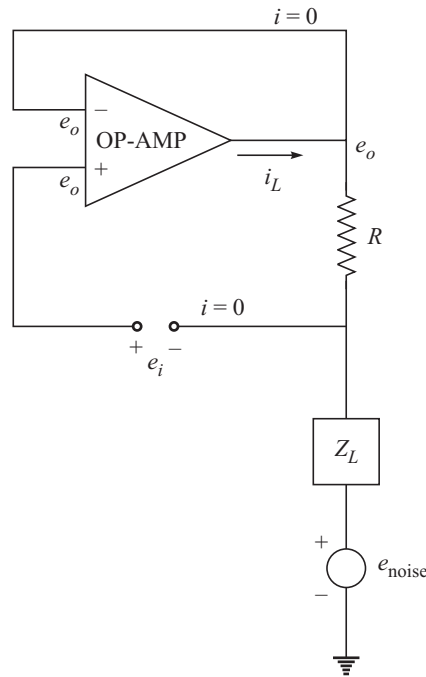


Fig. 1 Basic op-amp current source (Fig. 10.3)

The op-amp strives to maintain the positive and negative amplifier inputs equal, by adjusting e_o , the negative input is directly connected to e_o , so the positive input will also be at the same value because of the very high op-amp gain. Also, the current into each of the amplifier inputs is negligibly small. Since

the positive input terminal and the output terminal are at the same voltage, a loop through them, R and e_i results in $i_L = e_i/R$. This will hold even if there is a “noise voltage” present that changes the potential at the “bottom” of the load impedance Z_L . If there is any change in the noise voltage of load, the op-amp would change e_o to bring the load current back to the value commanded by e_i .