

## Laboratory Application Assignment

In this lab application assignment you will examine the difference between a linear and nonlinear resistance. Recall from your reading that a linear resistance has a constant value of ohms. Conversely, a nonlinear resistance has an ohmic value that varies with different amounts of voltage and current.

**Equipment:** Obtain the following items from your instructor.

- Variable DC power supply
- DMM
- 330- $\Omega$  and 1 k $\Omega$  carbon-film resistors ( $\frac{1}{2}$ -W)
- 12-V incandescent bulb

### Linear Resistance

Measure and record the value of the 330- $\Omega$  carbon-film resistor.  $R =$  \_\_\_\_\_

Connect the circuit in Fig. 3-18. Measure and record the current,  $I$ , with the voltage,  $V$ , set to 3 V.  $I =$  \_\_\_\_\_

Increase the voltage to 6 V and remeasure the current,  $I$ .  $I =$  \_\_\_\_\_

Increase the voltage one more time to 12 V, and remeasure the current,  $I$ .  $I =$  \_\_\_\_\_

For each value of voltage and current, calculate the resistance value as  $R = V/I$ . When  $V = 3$  V,  $R =$  \_\_\_\_\_. When  $V = 6$  V,

$R =$  \_\_\_\_\_. When  $V = 12$  V,  $R =$  \_\_\_\_\_. Does  $R$  remain the same even though  $V$  and  $I$  are changing? \_\_\_\_\_

### Nonlinear Resistance

Measure and record the cold resistance of the 12-V incandescent bulb.  $R =$  \_\_\_\_\_

In Fig. 3-18 replace the 330- $\Omega$  carbon-film resistor with the 12-V incandescent bulb.

Measure and record the current,  $I$ , with the voltage,  $V$ , set to 3 V.  $I =$  \_\_\_\_\_

Increase the voltage to 6 V, and remeasure the current,  $I$ .  $I =$  \_\_\_\_\_

Increase the voltage one more time to 12 V, and remeasure the current,  $I$ .  $I =$  \_\_\_\_\_

Calculate the resistance of the bulb as  $R = V/I$  for each value of applied voltage. When  $V = 3$  V,  $R =$  \_\_\_\_\_. When  $V = 6$  V,  $R =$  \_\_\_\_\_. When  $V = 12$  V,  $R =$  \_\_\_\_\_.

Does  $R$  remain constant as the values of voltage and current increase? \_\_\_\_\_

Does the bulb's resistance increase or decrease as  $V$  and  $I$  increase? \_\_\_\_\_

### Calculating Power

(330- $\Omega$  resistor)

Calculate the power dissipated by the 330- $\Omega$  resistor with  $V = 3$  V.  $P =$  \_\_\_\_\_ W

Calculate the power dissipated by the 330- $\Omega$  resistor with  $V = 6$  V.  $P =$  \_\_\_\_\_ W

Calculate the power dissipated by the 330- $\Omega$  resistor with  $V = 12$  V.  $P =$  \_\_\_\_\_ W

What happens to the power dissipation each time the voltage,  $V$ , is doubled?

\_\_\_\_\_  
(12-V incandescent bulb)

Calculate the power dissipated by the 12-V incandescent bulb with  $V = 3$  V.  $P =$  \_\_\_\_\_ W

Calculate the power dissipated by the 12-V incandescent bulb with  $V = 6$  V.  $P =$  \_\_\_\_\_ W

Calculate the power dissipated by the 12-V incandescent bulb with  $V = 12$  V.  $P =$  \_\_\_\_\_ W

What happens to the power dissipation each time the voltage,  $V$ , is doubled?

How do the changes in power dissipation when  $V$  is doubled compare to the results obtained with the 330- $\Omega$  resistor? \_\_\_\_\_

### Volt-Ampere Characteristic of $R$

In Fig. 3-18, replace the 12-V incandescent bulb with a 1 k $\Omega$  resistor. Measure the current,  $I$  as the voltage,  $V$  is increased in 1 V increments from 0 to 12 V. Create a table to record your answers. From the data recorded in your table, draw a graph of the  $V$  and  $I$  values. This graph represents the volt-ampere characteristic of the 1 k $\Omega$   $R$ .

Reconnect the 12-V incandescent bulb in Fig. 3-18. Measure the current,  $I$  as the voltage,  $V$  is increased in 1 V increments from 0 to 12 V. Create a second table to record your answers. From the data recorded in your table, draw a graph of the  $V$  and  $I$  values. This graph represents the volt-ampere characteristic of the 12-V incandescent bulb.

How does the volt-ampere characteristic of the 1 k $\Omega$  resistor compare to that of the 12-V incandescent bulb? \_\_\_\_\_

Does the 12-V incandescent bulb have a linear or nonlinear resistance? \_\_\_\_\_

Explain your answer. \_\_\_\_\_

Figure 3-18

