

Laboratory Application Assignment

In this lab application assignment you will examine the characteristics of a simple series circuit. You will also troubleshoot a series with open and shorted resistors.

Equipment: Obtain the following items from your instructor.


- Variable DC power supply
- Assortment of carbon-film resistors
- DMM

Series Circuit Characteristics

Examine the series circuit in Fig. 4–51. Calculate and record the following values:

$R_T = \underline{\hspace{1cm}}$, $I = \underline{\hspace{1cm}}$, $V_1 = \underline{\hspace{1cm}}$, $V_2 = \underline{\hspace{1cm}}$, $V_3 = \underline{\hspace{1cm}}$

Figure 4–51

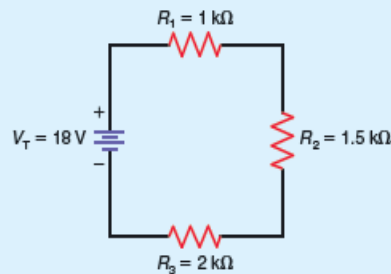

Construct the series circuit in Fig. 4–51. Measure and record the following values.

(Note that the power supply connections must be removed to measure R_T .)

$R_T = \underline{\hspace{1cm}}$, $I = \underline{\hspace{1cm}}$, $V_1 = \underline{\hspace{1cm}}$, $V_2 = \underline{\hspace{1cm}}$, $V_3 = \underline{\hspace{1cm}}$

How does the ratio V_2/V_1 compare to the ratio R_2/R_1 ? $\underline{\hspace{2cm}}$

How does the ratio V_3/V_1 compare to the ratio R_3/R_1 ? $\underline{\hspace{2cm}}$

Add the measured voltages V_1 , V_2 , and V_3 . Record your answer.

$\underline{\hspace{2cm}}$
How does this value compare to the value of V_T ? $\underline{\hspace{2cm}}$

Does the sum of the resistor voltage drops satisfy KVL? $\underline{\hspace{2cm}}$

Using measured values, prove that the current, I , is the same in all parts of a series circuit. Show your calculations. $\underline{\hspace{2cm}}$

$\underline{\hspace{2cm}}$

In Fig. 4–51, which series resistor dissipates the most amount of power? $\underline{\hspace{2cm}}$

Which resistor dissipates the least amount of power? $\underline{\hspace{2cm}}$

Troubleshooting a Series Circuit

In the following troubleshooting exercise, a $1\text{ }\Omega$ resistor will be used to simulate a short circuit whereas a $1\text{ M}\Omega$ resistor will be used to simulate an open circuit.

In Fig. 4–51, replace resistor R_2 with a $1\text{ }\Omega$ resistor. Next, measure and record the current, I and the voltages V_1 , V_2 and V_3 .
 $I = \underline{\hspace{1cm}}$, $V_1 = \underline{\hspace{1cm}}$, $V_2 = \underline{\hspace{1cm}}$, $V_3 = \underline{\hspace{1cm}}$

Did the current, I , increase or decrease with R_2 shorted? $\underline{\hspace{2cm}}$
Explain why. $\underline{\hspace{2cm}}$

Did the voltage drops across R_1 and R_3 increase or decrease with R_2 shorted? $\underline{\hspace{2cm}}$
Explain why. $\underline{\hspace{2cm}}$

Did the voltage drop across R_2 increase or decrease with R_2 shorted? $\underline{\hspace{2cm}}$
Explain why. $\underline{\hspace{2cm}}$

Next, change R_2 to a $1\text{ M}\Omega$ resistor. Measure and record the current, I and the voltages V_1 , V_2 and V_3 .

$I = \underline{\hspace{1cm}}$, $V_1 = \underline{\hspace{1cm}}$, $V_2 = \underline{\hspace{1cm}}$, $V_3 = \underline{\hspace{1cm}}$

Did the current, I increase or decrease with R_2 open? $\underline{\hspace{2cm}}$
Explain why. $\underline{\hspace{2cm}}$

Did the voltage drops across R_1 and R_3 increase or decrease with R_2 open? $\underline{\hspace{2cm}}$
Explain why. $\underline{\hspace{2cm}}$

Did the voltage drop across R_2 increase or decrease with R_2 open? $\underline{\hspace{2cm}}$
Explain why. $\underline{\hspace{2cm}}$

$\underline{\hspace{2cm}}$

$\underline{\hspace{2cm}}$