

Laboratory Application Assignment

In this lab application assignment you will examine how the capacitive reactance, X_C , of a capacitor decreases when the frequency, f , increases. You will also see that more capacitance, C , at a given frequency results in less capacitive reactance, X_C . Finally, you will observe how X_C values combine in series and in parallel.

Equipment: Obtain the following items from your instructor.

- Function generator
- Assortment of capacitors
- DMM

Capacitive Reactance, X_C

Refer to Fig. 17-18a. Calculate and record the value of X_C for each of the following frequencies listed below. Calculate X_C as $1/(2\pi fC)$.

$$X_C = \text{_____} @ f = 100 \text{ Hz}$$

$$X_C = \text{_____} @ f = 200 \text{ Hz}$$

$$X_C = \text{_____} @ f = 400 \text{ Hz}$$

Connect the circuit in Fig. 17-18a. Set the voltage source to exactly $5 V_{\text{rms}}$. For each of the following frequencies listed below, measure and record the current, I . (Use a DMM to measure I .) Next, calculate X_C as V/I .

$$I = \text{_____} @ f = 100 \text{ Hz}; X_C = \text{_____}$$

$$I = \text{_____} @ f = 200 \text{ Hz}; X_C = \text{_____}$$

$$I = \text{_____} @ f = 400 \text{ Hz}; X_C = \text{_____}$$

How do the experimental values of X_C compare to those initially calculated? _____

Based on your experimental values, what happens to the value of X_C each time the frequency, f , is doubled? _____

Is X_C proportional or inversely proportional to the frequency, f ? _____

Refer to Fig. 17-18b. With the frequency, f , set to 500 Hz, calculate and record the value of X_C for each of the following capacitance values listed below. Calculate X_C as $1/(2\pi fC)$.

$$X_C = \text{_____} \text{ when } C = 0.1 \mu\text{F}$$

$$X_C = \text{_____} \text{ when } C = 0.22 \mu\text{F}$$

$$X_C = \text{_____} \text{ when } C = 0.47 \mu\text{F}$$


Connect the circuit in Fig. 17-18b. Adjust the frequency of the function generator to exactly 500 Hz. For each of the following capacitance values listed below, measure and record the current, I . (Use a DMM to measure I .) Next, calculate X_C as V/I .

$$I = \text{_____} \text{ when } C = 0.1 \mu\text{F}; X_C = \text{_____}$$


$$I = \text{_____} \text{ when } C = 0.22 \mu\text{F}; X_C = \text{_____}$$

$$I = \text{_____} \text{ when } C = 0.47 \mu\text{F}; X_C = \text{_____}$$

Figure 17-18

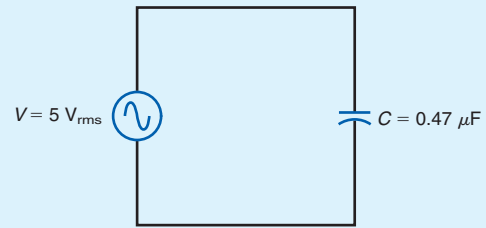

(a)

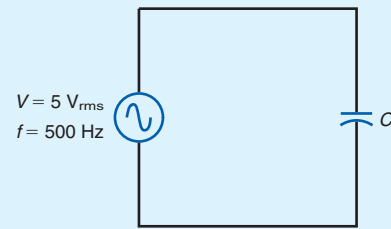

(b)

Is X_C proportional or inversely proportional to the value of capacitance? _____

Series Capacitive Reactances

Refer to the circuit in Fig. 17-19a. Calculate and record the following values:

$$X_{C1} = \text{_____}, X_{C2} = \text{_____}, X_{Ct} = \text{_____}, I = \text{_____},$$

$$V_{C1} = \text{_____}, V_{C2} = \text{_____}$$

Do V_{C1} and V_{C2} add to equal V_t ? _____

Construct the circuit in Fig. 17-19a. Set the frequency of the function generator to exactly 500 Hz. Next, using a DMM, measure and record the following values:

$$I = \text{_____}, V_{C1} = \text{_____}, V_{C2} = \text{_____}$$

Using the measured values of voltage and current, calculate the following values:

$$X_{C1} = \text{_____}, X_{C2} = \text{_____}, X_{Ct} = \text{_____}$$

Are the experimental values calculated here close to those initially calculated above? _____

Parallel Capacitive Reactances

Refer to the circuit in Fig. 17-19b. Calculate and record the following values:

$$X_{C1} = \text{_____}, X_{C2} = \text{_____}, I_{C1} = \text{_____}, I_{C2} = \text{_____},$$

$$I_t = \text{_____}, X_{Ct} = \text{_____}$$

Do I_{C_1} and I_{C_2} add to equal I_T ? _____

Construct the circuit in Fig. 17-19b. Set the frequency of the function generator to exactly 500 Hz. Next, using a DMM, measure and record the following values:

$I_{C_1} =$ _____, $I_{C_2} =$ _____, $I_T =$ _____

Using the measured values of voltage and current, calculate the following values:

$X_{C_1} =$ _____, $X_{C_2} =$ _____, $X_{C_{eq}} =$ _____

Are the experimental values calculated here close to those initially calculated above? _____

Figure 17-19

