

Laboratory Application Assignment

In this lab application assignment you will examine how the inductive reactance, X_L , of an inductor increases when the frequency, f , increases. You will also see that more inductance, L , at a given frequency results in more inductive reactance, X_L . Finally, you will observe how X_L values combine in series and in parallel.

Equipment: Obtain the following items from your instructor.

- Function generator
- 33-mH and 100-mH inductors
- DMM

DC Resistance, r_i , of a Coil

With a DMM, measure and record the dc resistance of each inductor. Set the DMM to the lowest resistance range when measuring r_i .

$$r_i = \text{_____} (33 \text{ mH})$$
$$r_i = \text{_____} (100 \text{ mH})$$

Inductive Reactance, X_L

Refer to Fig. 20–17a. Calculate and record the value of X_L for each of the following frequencies listed below. Calculate X_L as $2\pi fL$.

$$X_L = \text{_____} @ f = 500 \text{ Hz}$$
$$X_L = \text{_____} @ f = 1 \text{ kHz}$$
$$X_L = \text{_____} @ f = 2 \text{ kHz}$$

Connect the circuit in Fig. 20–17a. Set the voltage source to exactly 5 Vrms. For each of the following frequencies listed below, measure and record the current, I . (Use a DMM to measure I .) Next, calculate X_L as V/I .



$$I = \text{_____} @ f = 500 \text{ Hz}; X_L = \text{_____}$$
$$I = \text{_____} @ f = 1 \text{ kHz}; X_L = \text{_____}$$
$$I = \text{_____} @ f = 2 \text{ kHz}; X_L = \text{_____}$$

How do the experimental values of X_L compare to the calculated values? _____

Based on your experimental values, what happens to the value of X_L every time the frequency, f , doubles? _____

Is X_L proportional or inversely proportional to the frequency, f ? _____

Figure 20–17

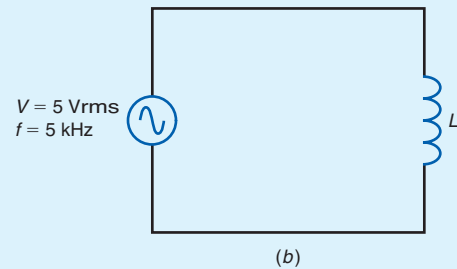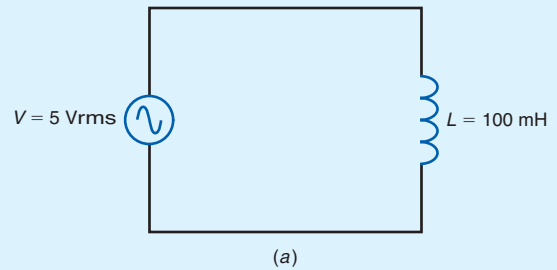

Refer to Fig. 20–17b. With the frequency, f , set to 5 kHz, calculate and record the value of X_L for each of the following inductance values listed below. Calculate X_L as $2\pi fL$.

$$X_L = \text{_____} \text{ when } L = 33 \text{ mH}$$
$$X_L = \text{_____} \text{ when } L = 100 \text{ mH}$$

Connect the circuit in Fig. 20–17b. Adjust the frequency, f , of the function generator to exactly 5 kHz. For each inductance value listed below, measure and record the current, I . (Use a DMM to measure I .) Next, calculate X_L as V/I .

$$I = \text{_____} \text{ when } L = 33 \text{ mH}; X_L = \text{_____}$$
$$I = \text{_____} \text{ when } L = 100 \text{ mH}; X_L = \text{_____}$$

Is X_L proportional or inversely proportional to the value of inductance? _____

Did the dc resistance, r_i , of the inductors affect any of your measurements? _____

If so, explain. _____

Series Inductive Reactances

Refer to the circuit in Fig. 20–18a. Calculate and record the following values:

$$X_{L_1} = \underline{\hspace{2cm}}, X_{L_2} = \underline{\hspace{2cm}}, X_{L_T} = \underline{\hspace{2cm}},$$

$$I = \underline{\hspace{2cm}}, V_{L_1} = \underline{\hspace{2cm}}, V_{L_2} = \underline{\hspace{2cm}}$$

Do V_{L_1} and V_{L_2} add to equal V_T ? $\underline{\hspace{2cm}}$

Construct the circuit in Fig. 20–18a. Set the frequency of the function generator to exactly 5 kHz. Next, using a DMM, measure and record the following values:

$$I = \underline{\hspace{2cm}}, V_{L_1} = \underline{\hspace{2cm}}, V_{L_2} = \underline{\hspace{2cm}}$$

Using the measured values of voltage and current, calculate the following values:

$$X_{L_1} = \underline{\hspace{2cm}}, X_{L_2} = \underline{\hspace{2cm}}, X_{L_T} = \underline{\hspace{2cm}}$$

Are the experimental values calculated here close to those initially calculated? $\underline{\hspace{2cm}}$

Parallel Inductive Reactances

Refer to the circuit in Fig. 20–18b. Calculate and record the following values:

$$X_{L_1} = \underline{\hspace{2cm}}, X_{L_2} = \underline{\hspace{2cm}}, I_{L_1} = \underline{\hspace{2cm}},$$

$$I_{L_2} = \underline{\hspace{2cm}}, I_T = \underline{\hspace{2cm}}, X_{L_{eq}} = \underline{\hspace{2cm}}$$

Do I_{L_1} and I_{L_2} add to equal I_T ? $\underline{\hspace{2cm}}$

Construct the circuit in Fig. 20–18b. Set the frequency of the function generator to exactly 5 kHz. Next, using a DMM, measure and record the following values:

$$I_{L_1} = \underline{\hspace{2cm}}, I_{L_2} = \underline{\hspace{2cm}}, I_T = \underline{\hspace{2cm}}$$

Using the measured values of voltage and current, calculate the following values:

$$X_{L_1} = \underline{\hspace{2cm}}, X_{L_2} = \underline{\hspace{2cm}}, X_{L_{eq}} = \underline{\hspace{2cm}}$$

Are the experimental values calculated here similar to those initially calculated? $\underline{\hspace{2cm}}$

Figure 20–18

