

Laboratory Application Assignment

In this lab application assignment you will examine the real power, apparent power, and power factor (PF) in a parallel RL circuit. You will also examine how a capacitor can be added in parallel to bring the power factor closer to 1 or unity. The procedure of adding a capacitor in parallel to raise the power factor is called power factor correction.

Note: In this lab we will assume that the dc resistance, r_l , of the inductor is negligible.

Equipment: Obtain the following items from your instructor.

- Function generator
- Oscilloscope
- DMM
- 100-mH inductor
- 0.22- μ F capacitor
- 10- Ω and 680- Ω resistors

Real Power, Apparent Power, and Power Factor

Examine the parallel RL circuit in Fig. 23-34a. (Ignore the 0.22- μ F capacitor.) Calculate and record the following circuit values:

$X_L = \underline{\hspace{2cm}}$, $I_L = \underline{\hspace{2cm}}$, $I_R = \underline{\hspace{2cm}}$,
 $I_T = \underline{\hspace{2cm}}$, $Z_{EQ} = \underline{\hspace{2cm}}$,
 $\theta_i = \underline{\hspace{2cm}}$, real power = $\underline{\hspace{2cm}}$,
 apparent power = $\underline{\hspace{2cm}}$, PF = $\underline{\hspace{2cm}}$

Construct the circuit in Fig. 23-34a. (Again, ignore the 0.22- μ F capacitor.)

Adjust the applied voltage, V_A , to exactly 5 Vrms. With a DMM, measure and record the following circuit values:

$I_L = \underline{\hspace{2cm}}$, $I_R = \underline{\hspace{2cm}}$,
 $I_T = \underline{\hspace{2cm}}$

Using the measured values of I_L and I_R , calculate the total current, I_T as $I_T = \sqrt{I_R^2 + I_L^2}$. Does this value agree with the measured value of total current? $\underline{\hspace{2cm}}$ If not, list one possible reason why. $\underline{\hspace{2cm}}$

Using the measured values of I_L and I_R , calculate the circuit's phase angle, θ_i . (Recall that in a parallel circuit, $\tan \theta_i = -I_L/I_R$.) $\theta_i = \underline{\hspace{2cm}}$. Next, using measured values, determine the following: real power = $\underline{\hspace{2cm}}$, apparent power = $\underline{\hspace{2cm}}$, PF = $\underline{\hspace{2cm}}$. How do these experimental values compare to those initially calculated? $\underline{\hspace{2cm}}$

Power Factor Correction

Mentally connect the 0.22- μ F capacitor in Fig. 23-34a.


Calculate and record the following circuit values:

$X_L = \underline{\hspace{2cm}}$, $X_C = \underline{\hspace{2cm}}$, $I_L = \underline{\hspace{2cm}}$,
 $I_C = \underline{\hspace{2cm}}$, $I_X = \underline{\hspace{2cm}}$,
 $I_R = \underline{\hspace{2cm}}$, $I_T = \underline{\hspace{2cm}}$, $Z_{EQ} = \underline{\hspace{2cm}}$,
 $\theta_i = \underline{\hspace{2cm}}$, apparent power = $\underline{\hspace{2cm}}$,
 real power = $\underline{\hspace{2cm}}$, PF = $\underline{\hspace{2cm}}$

Construct the circuit in Fig. 23-34a including the 0.22- μ F capacitor. Adjust the applied voltage, V_A , to exactly 5 Vrms. With a DMM, measure and record the following circuit values:

$I_L = \underline{\hspace{2cm}}$, $I_C = \underline{\hspace{2cm}}$,
 $I_R = \underline{\hspace{2cm}}$, $I_T = \underline{\hspace{2cm}}$

Figure 23-34

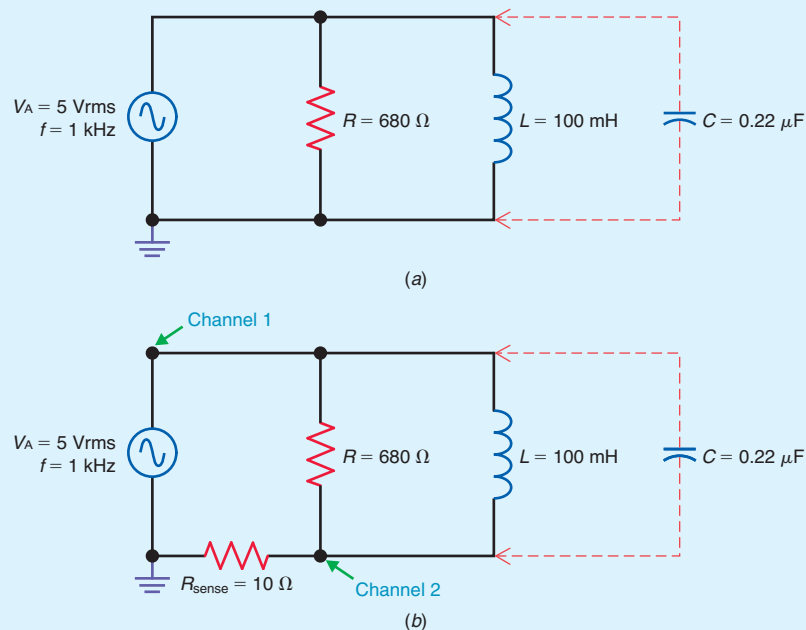

While measuring the total current, I_T , connect and disconnect the 0.22- μF capacitor several times. You should notice that I_T decreases when the capacitor is connected. Explain why this happens. _____

Using measured values, calculate the net reactive current, I_X , as $I_L - I_C$ or $I_C - I_L$ depending on which current is larger.

$I_X =$ _____

Using the experimental value of I_X and the measured value of I_R , calculate the circuit's phase angle, θ_I . $\theta_I =$ _____

Using measured values, calculate the following:

apparent power = _____, real power = _____,

PF = _____

In Figure 23-34a

a. Did the apparent power increase, decrease, or stay the same when the capacitor was added? _____

b. Did the phase angle, θ_I , become more negative, less negative, or did it stay the same when the capacitor was added? _____

c. Did the real power increase, decrease, or stay the same when the capacitor was added? _____

d. Did the power factor, PF, increase, decrease, or stay the same when the capacitor was added? _____

Add a 10- Ω sensing resistor as shown in Fig. 23-34b. Next, connect the oscilloscope to measure the phase angle, θ_I , between V_A and I_T . Note the connections designated for channels 1 and 2 in the figure. While viewing the displayed waveforms on the oscilloscope, connect and disconnect the 0.22- μF capacitor several times. Explain what happens to the phase angle when the capacitor is connected. _____