

Laboratory Application Assignment

In this lab application assignment you will examine the resonant effect in both series and parallel LC circuits. You will construct a series LC circuit and see how the current, I , rises to its maximum value at resonance. You will also construct a parallel LC circuit and see how the impedance, Z , rises to its maximum value at resonance.

Equipment: Obtain the following items from your instructor.

- Function generator
- Oscilloscope
- 4.7-mH inductor
- 0.001- μ F capacitor
- 47- Ω and 100 k Ω carbon-film resistors

Determining the Resonant Frequency, f_r , of a Series LC Circuit

Examine the series LC circuit in Fig. 25-22a. Calculate and record the resonant frequency, f_r . $f_r =$ _____

Construct the series LC circuit in Fig. 25-22a. Connect channel 1 of the oscilloscope to the input voltage, V_{in} , and channel 2 across the resistor, R , as shown. Set the input voltage



to 1 V_{p-p} and the frequency, f , to the value calculated for f_r . While viewing the resistor voltage, V_R , move the frequency dial back and forth. Measure and record the frequency that produces the maximum resistor voltage, V_R . This frequency is the resonant frequency, f_r . $f_r =$ _____

Record the measured value of V_R at f_r . (Make sure that V_{in} is still set to 1 V_{p-p} .) $V_R =$ _____ Does the fact that V_R is maximum at f_r prove that the series current, I , is also maximum at f_r ? _____ If your answer was yes, then explain why. _____

Using the measured value of V_R , calculate and record the series current, I , at f_r [$I = V_{R(p-p)}/R$]. $I =$ _____ p.p. Based on the fact that the current, I , decreases to 70.7% of its maximum value at the edge frequencies f_1 and f_2 , experimentally determine the bandwidth, Δf , of the resonant circuit. (This may be difficult to do.) $\Delta f =$ _____ Calculate the Q of the circuit using the measured values of f_r and Δf . $Q =$ _____

Using the oscilloscope, measure and record the phase relationship between V_{in} and V_R at f_r . $\theta =$ _____

Figure 25-22

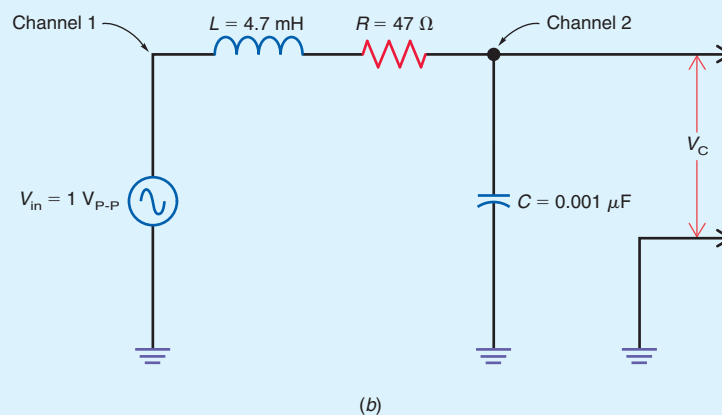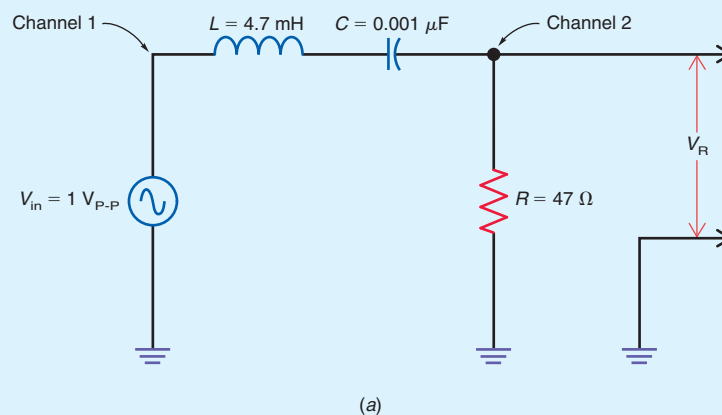

Does the series current have the same phase as the resistor voltage, V_R ? _____. If so, what is the phase relationship between V_{in} and I at f_r ? $\theta =$ _____

While adjusting the frequency dial above and below resonance, does the input voltage, V_{in} , dip at the resonant frequency? _____. If your answer was yes, explain why this occurs. _____

Rearrange the components as in Fig. 25-22b. Move the frequency dial back and forth until the capacitor voltage, V_C , is at its maximum value. The frequency at which V_C is maximum is the resonant frequency, f_r . This frequency should be very close to the frequency where V_R was maximum in Fig. 25-22a. Record the peak-to-peak capacitor voltage, V_C . $V_C =$ _____ p.p. Is this value larger than the input voltage, V_{in} ? _____. If so, how is this possible? _____

Determining the Resonant Frequency, f_r , of a Parallel Resonant Circuit

Examine the parallel LC circuit in Fig. 25-23. Calculate and record the resonant frequency, f_r . $f_r =$ _____

Construct the parallel LC circuit in Fig. 25-23. Connect channel 1 of the oscilloscope to the input voltage, V_{in} , and channel 2 across the tank circuit. Set the input voltage to

10 V_{p-p} and the frequency, f , to the value calculated for f_r . While viewing the tank voltage, V_{tank} , move the frequency dial back and forth. Measure and record the frequency that produces the maximum tank voltage, V_{tank} . This frequency is the resonant frequency, f_r . $f_r =$ _____. Is the resonant frequency, f_r , the same as it was in Fig. 25-22? _____

Does this prove that the resonant frequency is calculated the same way for both series and parallel LC circuits? _____

In Fig. 25-23, why is the tank voltage, V_{tank} , maximum at f_r ? _____

From the measured values in Fig. 25-23, explain how the tank impedance, Z_{tank} , can be experimentally determined. _____

What is the value of the tank impedance in Fig. 25-23?

$Z_{tank} =$ _____

What is the measured phase relationship between V_{in} and V_{tank} at f_r ? _____

Does the input voltage, V_{in} , dip at the resonant frequency like it did in the series LC circuit of Fig. 25-22? _____. If not, explain why. _____

Figure 25-23

