

## Laboratory Application Assignment

In this lab application assignment you will examine an  $RC$  coupling circuit and an  $RC$  low-pass filter. In the  $RC$  coupling circuit you will see how the series capacitor blocks the dc component of the input voltage but passes the ac component. In the  $RC$  low-pass filter you will see how the low frequencies are passed from input to output with little or no attenuation but the higher frequencies are severely attenuated or blocked.

**Equipment:** Obtain the following items from your instructor.

- Function generator
- Oscilloscope
- DMM
- 0.1- $\mu\text{F}$  and 0.22- $\mu\text{F}$  capacitors
- 2.2-k $\Omega$  and 10-k $\Omega$  carbon-film resistors

### $RC$ Coupling Circuit

Examine the  $RC$  coupling circuit in Fig. 26-43a. Notice the input voltage is a pulsating dc voltage whose value remains entirely positive. The input waveform (across terminals 1 and 2) is shown in Fig. 26-43b. The output from the  $RC$  coupling circuit is taken across terminals 3 and 4, which is across the resistor,  $R$ .

What value of dc voltage would you expect to measure across input terminals 1 and 2?  $V_{\text{in(dc)}} =$  \_\_\_\_\_

What value of rms voltage would you expect to measure across input terminals 1 and 2?  $V_{\text{in(rms)}} =$  \_\_\_\_\_

How much dc voltage would you expect to measure across the capacitor,  $C$ ?  $V_{C(\text{dc})} =$  \_\_\_\_\_

How much dc voltage would you expect to measure across the resistor,  $R$ ?  $V_{R(\text{dc})} =$  \_\_\_\_\_

Construct the circuit in Fig. 26-43a. With a DMM connected to the output of the function generator, adjust the dc offset control to obtain a dc value of +5 V dc. Also, while viewing the oscilloscope, adjust the amplitude and frequency controls of the function generator to obtain an output voltage of 10 V<sub>p-p</sub> with a frequency of 1 kHz. Have your instructor check your settings.

Next, measure and record the following values in Fig. 26-43a:

$V_{\text{in(dc)}} =$  \_\_\_\_\_,  $V_{\text{in(rms)}} =$  \_\_\_\_\_,

$V_{C(\text{dc})} =$  \_\_\_\_\_,  $V_{R(\text{dc})} =$  \_\_\_\_\_

How do these values compare to those predicted? \_\_\_\_\_

In Fig. 26-43a, calculate  $X_C$  and  $Z_T$  at 1 kHz.  $X_C =$  \_\_\_\_\_,  $Z_T =$  \_\_\_\_\_


Next, calculate and record the following rms values:

$I =$  \_\_\_\_\_,  $V_C =$  \_\_\_\_\_,  $V_R =$  \_\_\_\_\_

Using your DMM, measure and record the following rms values:

$V_C =$  \_\_\_\_\_,  $V_R =$  \_\_\_\_\_

Figure 26-43

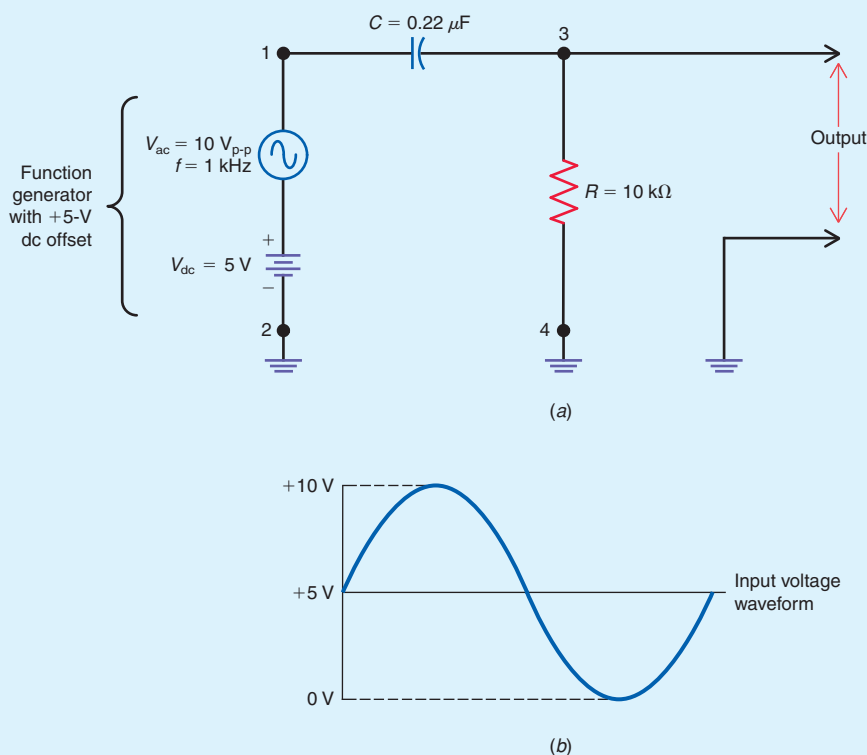

How do your calculated and measured rms values compare?

---

Measure and record the peak-to-peak output voltage across  $R$  using the oscilloscope.  $V_{\text{out}} = \text{_____ p.p.}$  How does this value compare to the peak-to-peak value of input voltage? \_\_\_\_\_

---

**RC Low-Pass Filter**

Examine the RC low-pass filter in Fig. 26-44. Calculate and record the cutoff frequency,  $f_c$ .  $f_c = \text{_____}$

Construct the RC low-pass filter in Fig. 26-44. The input voltage should be set to exactly 10 V<sub>p-p</sub> with no dc offset.

Measure and record the output voltage from the RC low-pass filter for each of the frequencies listed below. (Use the oscilloscope to measure the output voltage.) Next, calculate the decibel attenuation offered by the filter at each frequency.

$f = 100 \text{ Hz}$	$V_{\text{out(p-p)}} = \text{_____}$	$N_{\text{dB}} = \text{_____}$
$f = 250 \text{ Hz}$	$V_{\text{out(p-p)}} = \text{_____}$	$N_{\text{dB}} = \text{_____}$

$f = 500 \text{ Hz}$	$V_{\text{out(p-p)}} = \text{_____}$	$N_{\text{dB}} = \text{_____}$
$f_c \text{ (Calculated)}$	$V_{\text{out(p-p)}} = \text{_____}$	$N_{\text{dB}} = \text{_____}$
$f = 10 \text{ kHz}$	$V_{\text{out(p-p)}} = \text{_____}$	$N_{\text{dB}} = \text{_____}$
$f = 20 \text{ kHz}$	$V_{\text{out(p-p)}} = \text{_____}$	$N_{\text{dB}} = \text{_____}$
$f = 100 \text{ kHz}$	$V_{\text{out(p-p)}} = \text{_____}$	$N_{\text{dB}} = \text{_____}$

Do the measured values of output voltage confirm that the circuit is a low-pass filter? \_\_\_\_\_

**Rate of Rolloff**

Based on your measured values in Fig. 26-44, what is the rate of rolloff when  $f$  is increased by one octave from 10 kHz to 20 kHz?  
\_\_\_\_\_.

Based on your measured values in Fig. 26-44, what is the rate of rolloff when  $f$  is raised by one decade from 10 kHz to 100 kHz?  
\_\_\_\_\_.

**Figure 26-44**

