

Laboratory Application Assignment

In this lab application assignment you will examine two different biasing techniques used with transistors: base bias and voltage divider bias. You will see that with base bias, I_C and V_{CE} are beta-dependent values, whereas with voltage divider bias they are not.

Equipment: Obtain the following items from your instructor.

- Two 2N2222A *npn* transistors or equivalent
- DMM
- Assortment of carbon-film resistors
- Variable dc power supply

Beta, β_{dc}

Most handheld and bench-top DMMs available today are capable of measuring the dc beta of a transistor. If your DMM has this capability, measure and record the dc beta of each *npn* transistor supplied to you for this experiment. Keep each transistor separate.

$Q_1, \beta_{dc} =$ _____

$Q_2, \beta_{dc} =$ _____

Base Bias

Examine the circuit in Fig. 28–32. Calculate and record the following dc values for each of the two transistor betas:

Q_1

$I_B =$ _____

$I_C =$ _____

$V_{CE} =$ _____

Q_2

$I_B =$ _____

$I_C =$ _____

$V_{CE} =$ _____

Construct the circuit in Fig. 28–32. Measure and record the following dc values for each of the two transistors:

Q_1

$I_B =$ _____

$I_C =$ _____

$V_{CE} =$ _____


Q_2

$I_B =$ _____

$I_C =$ _____

$V_{CE} =$ _____

Figure 28–32

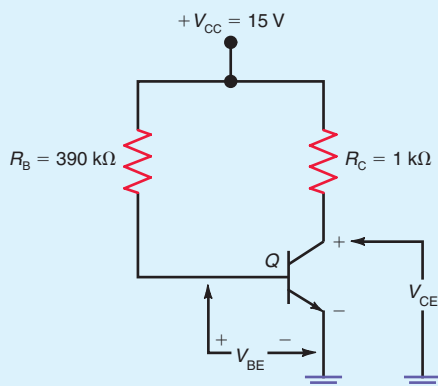

Voltage Divider Bias

Examine the circuit in Fig. 28–33. Calculate and record the following circuit values:

$V_B =$ _____

$V_C =$ _____

$V_E =$ _____

$V_{CE} =$ _____

$I_E =$ _____

Construct the circuit in Fig. 28–33. Measure the following circuit values using Q_1 as the transistor:

$V_B =$ _____

$V_C =$ _____

$V_E =$ _____

$V_{CE} =$ _____

$I_E =$ _____

Replace Q_1 with Q_2 and repeat the measurements listed.

$V_B =$ _____

$V_C =$ _____

$V_E =$ _____

$V_{CE} =$ _____

$I_E =$ _____

Which form of bias produces more stable results, base bias or voltage divider bias? _____ Explain your answer.

Figure 28–33

