

Laboratory Application Assignment

In this lab application assignment you will examine the ability of a transistor to amplify a small ac signal. You will build a common-emitter amplifier and measure the input and output voltages so you can determine the voltage gain, A_v . You will also see how the emitter bypass capacitor, C_E , and load resistance, R_L , affect the voltage gain, A_v .

Equipment: Obtain the following items from your instructor.

- 2N2222A *npn* transistor or equivalent
- Assortment of carbon-film resistors
- Two 100- μF electrolytic capacitors and one 220- μF electrolytic capacitor
- DMM
- Oscilloscope
- Function generator
- Variable dc power supply

Common-Emitter Amplifier Calculations

Examine the common-emitter amplifier in Fig. 29-26. Calculate and record the following dc quantities:

$V_B = \underline{\hspace{2cm}}, V_E = \underline{\hspace{2cm}}, I_E = \underline{\hspace{2cm}},$

$$V_C = \underline{\hspace{2cm}}, V_{CE} = \underline{\hspace{2cm}}$$

Next, calculate and record the following ac values with the emitter bypass capacitor, C_e , connected but *without* the load resistor, R_L . Note that $V_{in} = 10 \text{ mV}_{p-p}$.

$$r'_e = \underline{\hspace{2cm}}, A_V = \underline{\hspace{2cm}}, V_{out} = \underline{\hspace{2cm}}$$

Connect the load resistor, R_L , and recalculate A_V and V_{out} .

$$A_v = \underline{\hspace{2cm}}, V_{out} = \underline{\hspace{2cm}}$$

What happened to A_v and V_{out} when R_i was added? _____

With the load resistor, R_L , still connected, remove the emitter bypass capacitor, C_E , and recalculate A_v and V_{out} .

$$A_v = \underline{\hspace{2cm}}, V_{out} = \underline{\hspace{2cm}}$$

What happened to A_V and V_{out} when C_E was removed? _____

Common-Emitter Amplifier Measurements

Construct the common-emitter amplifier in Fig. 29–26. Adjust the input voltage, V_{in} , to exactly 10 mV_{p-p}. Measure and record the following dc quantities:

$$V_B = \underline{\hspace{2cm}}, V_E = \underline{\hspace{2cm}}, I_E = \underline{\hspace{2cm}},$$

$$V_C = \underline{\hspace{2cm}}, V_{CE} = \underline{\hspace{2cm}}$$

Next, measure and record the output voltage, V_{out} , with the emitter bypass capacitor, C_E , connected but *without the load* resistor, R_L . Using the measured value of V_{out} calculate the voltage gain, A_v .

$$V_{out} = \underline{\hspace{2cm}}, A_v = \underline{\hspace{2cm}}$$

Connect the load resistor, R_L , and remeasure V_{out} . Using the measured value of V_{out} , recalculate A_V .

$$A_v = \underline{\hspace{2cm}}, V_{out} = \underline{\hspace{2cm}}$$

What happened to V_{out} and A_v ? _____

With the load resistor, R_L , still connected, remove the emitter bypass capacitor, C_E , and remeasure V_{out} . Using the measured value of V_{out} , recalculate A_v .

$$V_{out} = \underline{\hspace{2cm}}, A_v = \underline{\hspace{2cm}}$$

Did A_V and V_{out} decrease substantially? _____ If yes, explain why. _____

Figure 29-26

