

Laboratory Application Assignment

In this lab application assignment you will examine a tuned class C amplifier. As you will see, the tuned class C amplifier uses a parallel resonant circuit in the collector, which results in maximum output voltage at only one frequency. The frequency at which maximum output occurs is the resonant frequency, f_r , of the LC tank circuit. You will also see how the tuned class C amplifier can be used as a frequency multiplier.

Equipment: Obtain the following items from your instructor.

- 2N2222A npn transistor or equivalent
- Two 100-k Ω carbon-film resistors
- 0.001- μ F, 0.01- μ F, and 0.1- μ F capacitors
- 10-mH inductor
- Function generator
- Oscilloscope
- DMM
- Variable dc power supply

Tuned Class C Amplifier: Calculations and Predictions

Examine the tuned class C amplifier in Fig. 31-16. Calculate and record the resonant frequency, f_r , of the LC tank circuit.

$f_r =$ _____

With an input voltage, V_{in} , of $2 V_{p-p}$, calculate and record the dc base voltage, V_B . $V_{B(dc)} =$ _____

What dc voltage do you expect to measure at the collector?


$V_{C(dc)} =$ _____

Next, predict the peak-to-peak output voltage across the load R_L if the frequency of V_{in} equals f_r . $V_{out(p-p)} =$ _____

Tuned Class C Amplifier: Measurements

Construct the circuit in Fig. 31-16. Set V_{in} to exactly $2 V_{p-p}$ as shown. Next, set the frequency of the function generator to the resonant frequency, f_r , calculated earlier. With channel 2 of the oscilloscope connected across the load, R_L , move the frequency dial back and forth until the output voltage is at its maximum

Figure 31-16

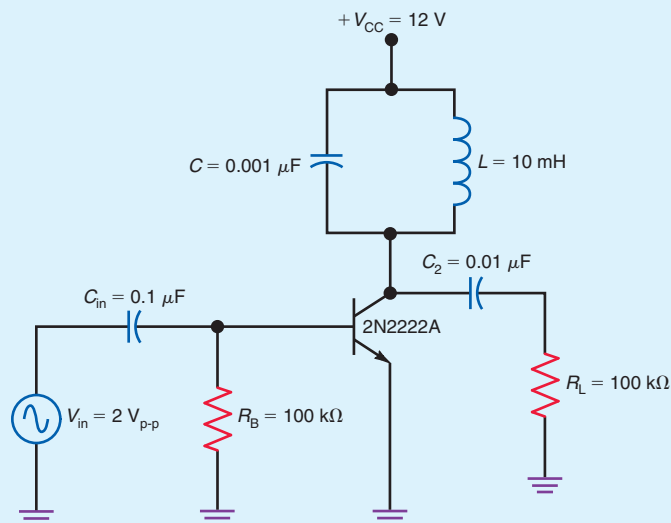

peak-to-peak value. Measure and record the frequency where $V_{out(p-p)}$ is maximum. This frequency is the resonant frequency, f_r , of the tank circuit. $f_r =$ _____


Measure and record the maximum peak-to-peak output voltage. $V_{out(p-p)} =$ _____

Next, measure and record the dc voltage at the base and collector. $V_{B(dc)} =$ _____, $V_{C(dc)} =$ _____

Connect channel 1 of the oscilloscope across V_{in} and channel 2 across the load, R_L . Measure and record the phase relationship between V_{in} and V_{out} at f_r . $\theta =$ _____

Connect channel 1 of the oscilloscope directly to the base of the transistor. Set the channel 1 volts/div. setting to 0.5 volt/div., and move the input coupling switch to dc. Draw the measured waveform, including all values, on the scope graticule in Fig. 31-17.

Figure 31-17

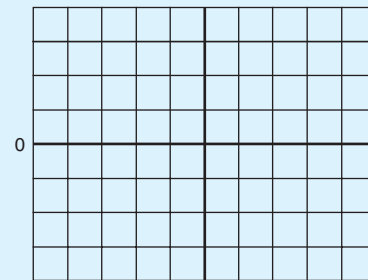

Amplifier Bandwidth

Reduce the input voltage, V_{in} , to $1.6 V_{p-p}$. While monitoring the peak-to-peak output voltage across R_L , decrease the frequency of V_{in} below f_r until the output voltage decreases to 0.707 of its maximum value. Record this frequency as f_1 .

$f_1 =$ _____

Now increase the frequency of V_{in} above f_r until V_{out} decreases to 0.707 of its maximum value. Record this frequency as f_2 .

$f_2 =$ _____

Calculate the amplifier bandwidth, BW, as $f_2 - f_1$.

BW = _____

Frequency Multiplier

Decrease the frequency of the function generator to approximately one-half of f_r . (Keep V_{in} at $1.6 V_{p-p}$.) Move the function generator frequency dial back and forth to produce the maximum peak-to-peak output voltage. Is the frequency of the output waveform twice that of the input frequency? _____
If yes, explain how this is possible. _____

Is the peak-to-peak value of the output waveform the same for each individual cycle? _____ If not, explain the possible cause for this. _____

