

Laboratory Application Assignment

In this lab application assignment you will examine how to properly test an SCR with an analog VOM. You will also see that a DMM cannot properly test an SCR. Finally, you will build a simple test circuit that reinforces the basic operation of an SCR.

Equipment: Obtain the following items from your instructor.

- Two SPST switches
- Simpson 260 analog VOM or equivalent
- DMM
- 12-V incandescent lamp
- Variable dc Power Supply
- 330- Ω carbon-film resistor
- Low- or medium-current SCR

Analog VOM

Examine the analog VOM you will be using for this part of the experiment. Set the VOM to the $R \times 1$ resistance range, and short the ohmmeter leads together. Adjust the zero-ohms control for full-scale deflection of the meter's pointer. If the pointer does not deflect all the way to 0 Ω , the meter's battery needs to be replaced. If this is the case, ask your instructor for a new battery.

Testing an SCR

With the analog VOM set to the $R \times 1$ range, connect the ohmmeter leads as shown in Fig. 32-16a. As you can see, this connection provides a positive (+) voltage at the anode (A) of the SCR with respect to the cathode (K). Even though the SCR is forward-biased, the forward voltage applied by the VOM is much less than the SCR's forward breakover voltage, V_{BRF} . Therefore, the meter should read infinite ohms, indicating that the SCR is *not* conducting. Does your meter show infinite ohms?




Reverse the connection of the ohmmeter leads as shown in Fig. 32-16b. As you can see, this connection reverse-biases the SCR because it applies a negative (–) voltage at the anode (A) with respect to the cathode (K). As a result, the meter should still read infinite ohms. Does it?

Return the ohmmeter leads to their original polarity as shown in Fig. 32-16c. With the gate lead still open, the meter should read infinite ohms. Now place a jumper from the anode (A) to the gate (G) as shown. This connection provides the gate with a positive (+) voltage with respect to the cathode (K). The meter should now read a low resistance. Does it?

If the meter shows a low resistance, it indicates the SCR is on or conducting.

Remove the jumper from the anode to the gate. The meter should still show a low resistance. Does it? Does this test indicate that once the SCR is conducting, the gate loses all control?

Figure 32-16

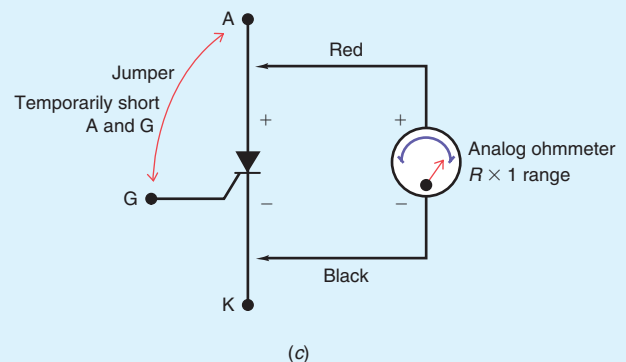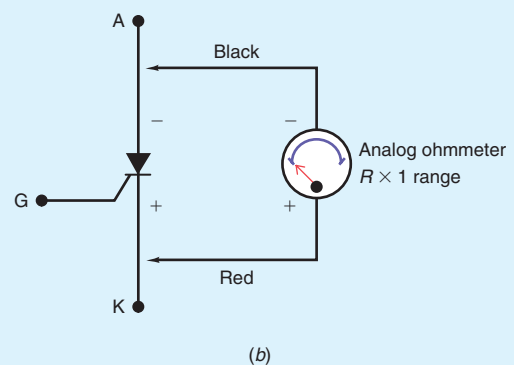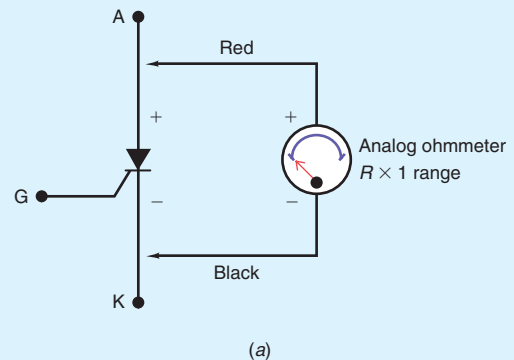

Do the results of your test indicate that the SCR is good or bad?

Repeat this testing procedure with a DMM. Pay special attention to the step where the jumper is removed from the anode to the gate. Describe, in detail, your results below.

SCR Test Circuit

Connect the SCR test circuit in Fig. 32-17. Switches S_1 and S_2 should initially be in the *open* position. Indicate the state of the lamp in each step of the following procedure.

a. With both S_1 and S_2 open, is the lamp lit or is it dark?

b. Close S_1 . Did the lamp light?

c. With S_1 still closed, now close S_2 . Is the lamp lit now?

d. Open S_2 . Did the lamp stay lit, or did it go dark?

e. Open S_1 . What is the condition of the lamp now?

In step d, did the SCR turn off when S_2 was opened? _____. If not, explain why.

Figure 32-17

