

Laboratory Application Assignment

In this lab application assignment you will examine two relatively simple op-amp circuits: the inverting and noninverting amplifier. In each amplifier circuit you will measure the output voltage, V_{out} , and determine the closed-loop voltage gain, A_{CL} , with different amounts of negative feedback. You will also measure the phase relationship between V_{in} and V_{out} in each type of amplifier.

Equipment: Obtain the following items from your instructor.

- Dual-output variable dc power supply
- Oscilloscope
- Function generator
- DMM
- 741C op amp
- Assortment of carbon-film resistors

Inverting Amplifier

Examine the inverting amplifier in Fig. 33-46. Calculate and record the closed-loop voltage gain, A_{CL} , and output voltage, V_{out} , for each of the following values of feedback resistance, R_F . Note that $V_{in} = 1\text{ V}_{p-p}$.

$R_F = 4.7\text{ k}\Omega$	$A_{CL} =$ _____	$V_{out(p-p)} =$ _____
$R_F = 10\text{ k}\Omega$	$A_{CL} =$ _____	$V_{out(p-p)} =$ _____
$R_F = 15\text{ k}\Omega$	$A_{CL} =$ _____	$V_{out(p-p)} =$ _____
$R_F = 22\text{ k}\Omega$	$A_{CL} =$ _____	$V_{out(p-p)} =$ _____

Construct the inverting amplifier in Fig. 33-46. (The IC pin numbers are shown in parentheses.) Set the input voltage, V_{in} , to exactly 1 V_{p-p} . Measure and record the output voltage, V_{out} , for each value of R_F listed below. Then from your measured values of V_{out} , calculate the closed-loop voltage gain, A_{CL} , as V_{out}/V_{in} .

$R_F = 4.7\text{ k}\Omega$	$V_{out(p-p)} =$ _____	$A_{CL} =$ _____
$R_F = 10\text{ k}\Omega$	$V_{out(p-p)} =$ _____	$A_{CL} =$ _____
$R_F = 15\text{ k}\Omega$	$V_{out(p-p)} =$ _____	$A_{CL} =$ _____
$R_F = 22\text{ k}\Omega$	$V_{out(p-p)} =$ _____	$A_{CL} =$ _____

How do your measured and calculated values compare? _____

With channel 1 of the oscilloscope connected to the input voltage, V_{in} , and channel 2 connected to the output of the op amp, measure and record the phase relationship between V_{in} and V_{out} . $\theta =$ _____

Measure and record the ac voltage at the inverting input (pin 2) of the op amp. $V_{(-)} =$ _____ V_{p-p} . Explain your measurement.

Noninverting Amplifier

Examine the noninverting amplifier in Fig. 33-47. Calculate and record the closed-loop voltage gain, A_{CL} , and output voltage, V_{out} , for each of the following values of feedback resistance, R_F . Note that $V_{in} = 1\text{ V}_{p-p}$.

$R_F = 1\text{ k}\Omega$	$A_{CL} =$ _____	$V_{out(p-p)} =$ _____
$R_F = 2\text{ k}\Omega$	$A_{CL} =$ _____	$V_{out(p-p)} =$ _____
$R_F = 10\text{ k}\Omega$	$A_{CL} =$ _____	$V_{out(p-p)} =$ _____
$R_F = 15\text{ k}\Omega$	$A_{CL} =$ _____	$V_{out(p-p)} =$ _____

Construct the noninverting amplifier in Fig. 33-47. (The IC pin numbers are shown in parentheses.) Set the input voltage, V_{in} , to exactly 1 V_{p-p} . Measure and record the output voltage, V_{out} , for each value of R_F listed below. Then from your measured values of V_{out} , calculate the closed-loop voltage gain, A_{CL} , as V_{out}/V_{in} .

$R_F = 1\text{ k}\Omega$	$V_{out(p-p)} =$ _____	$A_{CL} =$ _____
$R_F = 2\text{ k}\Omega$	$V_{out(p-p)} =$ _____	$A_{CL} =$ _____
$R_F = 10\text{ k}\Omega$	$V_{out(p-p)} =$ _____	$A_{CL} =$ _____
$R_F = 15\text{ k}\Omega$	$V_{out(p-p)} =$ _____	$A_{CL} =$ _____

How do your measured and calculated values compare? _____

With channel 1 of the oscilloscope connected to the input voltage, V_{in} , and channel 2 connected to the output of the op amp, measure and record the phase relationship between V_{in} and V_{out} . $\theta =$ _____

Figure 33-46


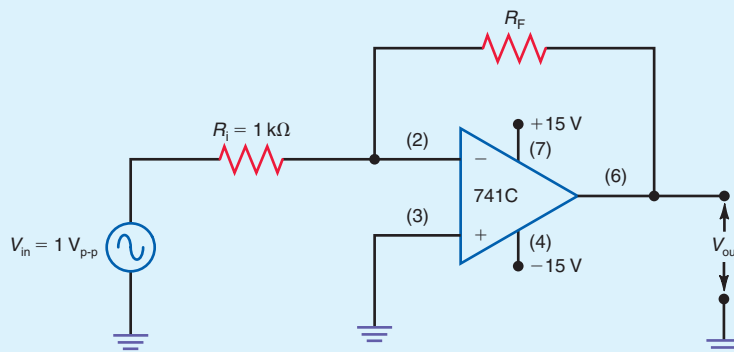


Figure 33-47

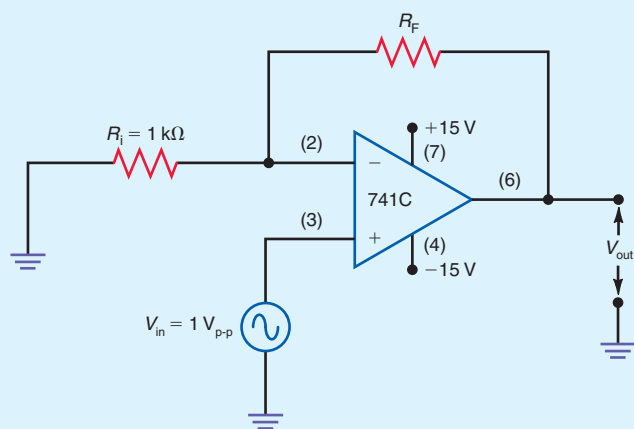

Measure and record the ac voltage at the noninverting input (pin 3) of the op amp. $V_{(+)} = \text{_____}_{p-p}$. Next, measure and record the ac voltage at the inverting input (pin 2) of the op amp. $V_{(-)} = \text{_____}_{p-p}$. Are these two values the same? _____ If yes, explain why. _____